

# CS2100

## Recitation 9

---

MSI Components  
24 March 2025  
Aaron Tan


# Contents

- Decoders
  - Implementing functions using decoders
  - Decoder with enable
  - Standard MSI decoder
- Encoders
  - Priority encoders
- Multiplexers
  - Standard MSI multiplexer
  - Implementing functions using multiplexers
  - Using smaller multiplexers
- Selected Past Years' Exam Questions
  - AY2016/17 Sem2 Q2
  - AY2017/18 Sem2 Q3(a)(b)(c)
  - AY2018/19 Sem2 Q5(c)
  - AY2019/20 Sem2 Q5(a)(b)


# SUMMARY

---


## Decoders

 

# Decoding – the inefficient way

 


# Decoding – the better way

 

## 2. Decoders (2/5)

 - Example: If codes 00, 01, 10, 11 are used to identify four persons, we may use a 2-bit decoder.




- This is a **2×4 decoder** which selects an output line based on the 2-bit code supplied.
- Truth table:

X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	<b>1</b>	0	0	0
0	1	0	<b>1</b>	0	0
1	0	0	0	<b>1</b>	0
1	1	0	0	0	<b>1</b>

## 2. Decoders (3/5)

- From truth table, circuit for **2×4 decoder** is:

X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	<b>1</b>	0	0	0
0	1	0	<b>1</b>	0	0
1	0	0	0	<b>1</b>	0
1	1	0	0	0	<b>1</b>

 


Each output is a **minterm** (X'·Y', X'·Y, X·Y' or X·Y) of a 2-variable function.

## 2. Decoders (4/5)

- Design a **3×8 decoder**.

x	y	z	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>
0	0	0	<b>1</b>	0	0	0	0	0	0	0
0	0	1	0	<b>1</b>	0	0	0	0	0	0
0	1	0	0	0	<b>1</b>	0	0	0	0	0
0	1	1	0	0	0	<b>1</b>	0	0	0	0
1	0	0	0	0	0	0	<b>1</b>	0	0	0
1	0	1	0	0	0	0	0	<b>1</b>	0	0
1	1	0	0	0	0	0	0	0	<b>1</b>	0
1	1	1	0	0	0	0	0	0	0	<b>1</b>

 

Each output is a **minterm** of a 3-variable function.



## 2. Decoders: Implementing Functions (1/3)


- A Boolean function, in **sum-of-minterms** form  $\Rightarrow$ 
  - decoder to generate the minterms, and
  - an OR gate to form the sum.
- Any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n:2^n$  decoder with  $m$  OR gates.
- Good when circuit has many outputs, and each function is expressed with a few minterms.

## 2. Decoders: Implementing Functions (2/3)

- Example: Full adder

$$S(x, y, z) = \Sigma m(1,2,4,7)$$

$$C(x, y, z) = \Sigma m(3,5,6,7)$$

 


<b>x</b>	<b>y</b>	<b>z</b>	<b>C</b>	<b>S</b>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## 2. Decoders: Implementing Functions (3/3)

$$S(x, y, z) = \Sigma m(1,2,4,7)$$

$$C(x, y, z) = \Sigma m(3,5,6,7)$$

 

**BRAVO!!!**


## 2. Decoders with Enable (1/2)

- Decoders often come with an **enable control** signal, so that the device is only activated when the enable,  $E = 1$ .

- Truth table:

E	X	Y	$F_0$	$F_1$	$F_2$	$F_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	d	d	0	0	0	0

 - Circuit of a **2×4 decoder with enable**:



## 2. Decoders with Enable (2/2)

- In the previous slide, the decoder has a **one-enable** control signal, i.e. the decoder is enabled with  $E=1$ .
- In most MSI decoders, enable signal is **zero-enable**, usually denoted by  $E'$  or  $\bar{E}$ . The decoder is enabled when the signal is zero (low).

E	X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	d	d	0	0	0	0



Decoder with 1-enable

E'	X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	d	d	0	0	0	0

Decoder with 0-enable

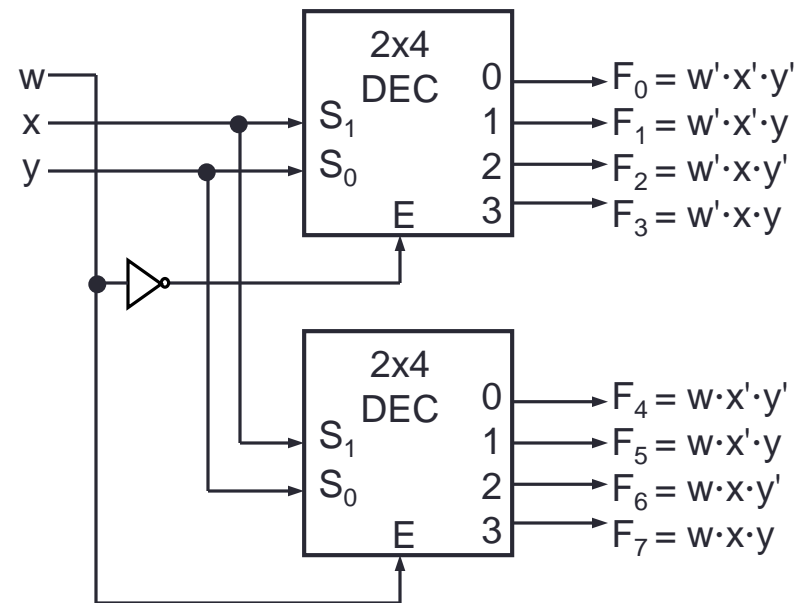
 
## 2. Constructing Larger Decoders (1/4)

- Larger decoders can be constructed from smaller ones.
- Example: A 3×8 decoder can be built from two 2×4 decoders (with one-enable) and an inverter.





## 2. Constructing Larger Decoders (2/4)

**BRAVO!!!**

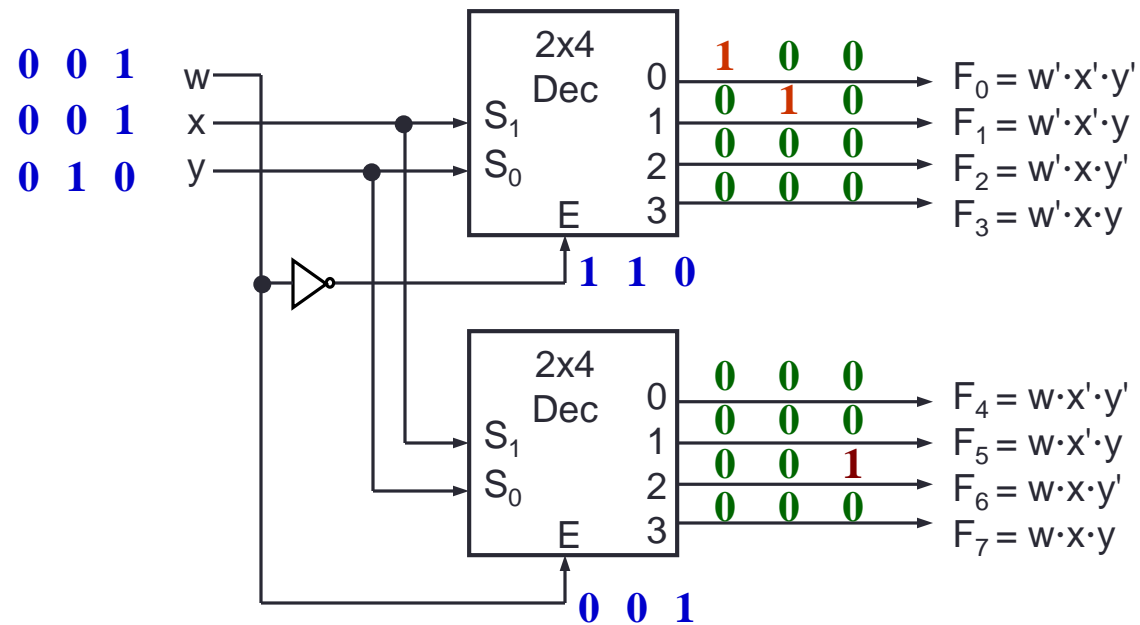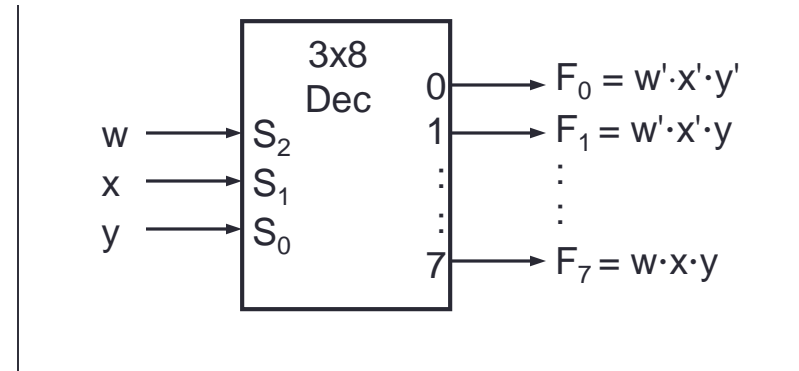
  
## 2. Constructing Larger Decoders (3/4)


- Construct a 4×16 decoder from two 3×8 decoders with one-enable and an inverter.



- Note: The input  $w$  and its complement  $w'$  are used to select either one of the two smaller decoders.



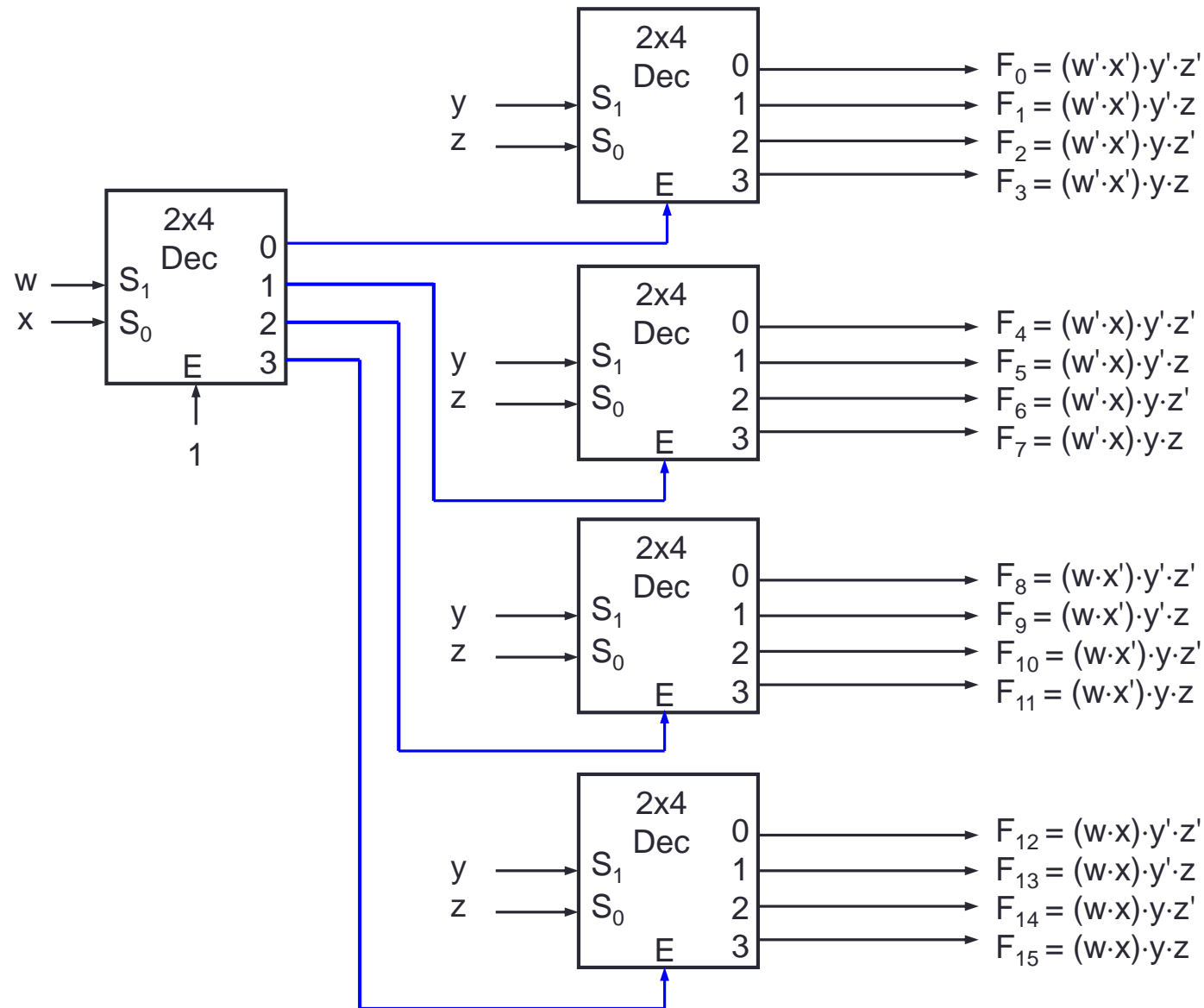**Exercise:** How to construct a 4×16 decoder using **five** 2×4 decoders with enable?



# Negated outputs (active low outputs) decoders

- A decoder may be 1-enabled or 0-enabled.
- A decoder may also normal output or **negated outputs**. (See next two slides.)
  - Normal outputs = active high outputs
  - Negated outputs = active low outputs

E	X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	d	d	0	0	0	0



1-enabled, active high  
outputs 2x4 decoder.

E	X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
1	0	0	0	1	1	1
1	0	1	1	0	1	1
1	1	0	1	1	0	1
1	1	1	1	1	1	0
0	d	d	1	1	1	1

1-enabled, active low  
outputs 2x4 decoder.

## 2. Standard MSI Decoder (1/2)

- 74138 (3-to-8 decoder)

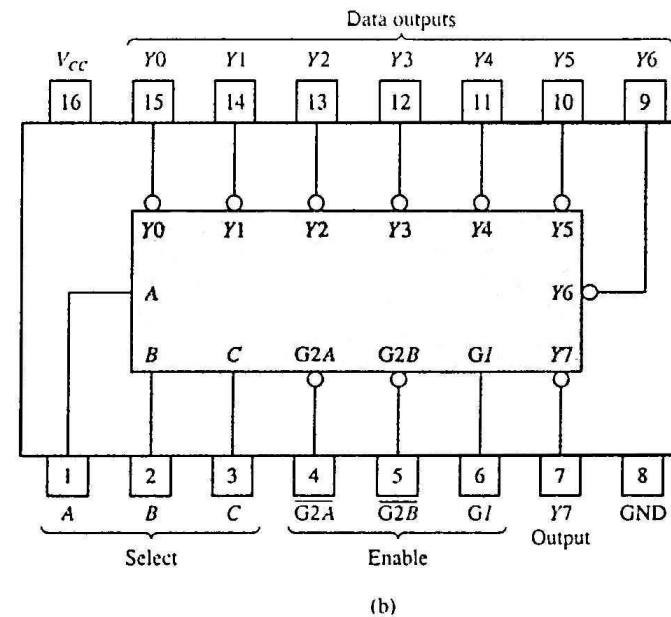 

74138 decoder module.

(a) Logic circuit.

(b) Package pin configuration.

## 2. Standard MSI Decoder (2/2)

INPUTS					OUTPUTS							
ENABLE		SELECT										
G1	$\overline{G2}^*$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	L	H	H	H	H
H	L	H	L	H	H	H	H	L	H	H	H	H
H	L	H	H	L	H	H	H	H	L	H	H	H
H	L	H	H	H	H	H	H	H	H	L	H	H

74138 decoder module.  
(c) Function table.

$$*\overline{G2} = \overline{G2A} + \overline{G2B}$$

H = high level, L = low level, X = irrelevant


(c)

74138 decoder module.


(d) Generic symbol.

 (e) IEEE standard logic symbol.

Source: *The Data Book Volume 2, Texas Instruments Inc., 1985*



(d)

 

(e)

## 2. Decoders: Implementing Functions Revisit (1/2)

- Example: Implement the following function using a 3×8 decoder and an appropriate logic gate


$$f(Q,X,P) = \sum m(0,1,4,6,7) = \prod M(2,3,5)$$

- We may implement the function in several ways:
  - Using a decoder with active-high outputs with an OR gate:
$$f(Q,X,P) = m_0 + m_1 + m_4 + m_6 + m_7$$
  - Using a decoder with active-low outputs with a NAND gate:
$$f(Q,X,P) = (m_0' \cdot m_1' \cdot m_4' \cdot m_6' \cdot m_7' )'$$
  - Using a decoder with active-high outputs with a NOR gate:
$$f(Q,X,P) = (m_2 + m_3 + m_5 )' [= M_2 \cdot M_3 \cdot M_5 ]$$
  - Using a decoder with active-low outputs with an AND gate:
$$f(Q,X,P) = m_2' \cdot m_3' \cdot m_5'$$


## 2. Decoders: Implementing Functions Revisit
 
### (2/2)


$$f(Q,X,P) = \sum m(0,1,4,6,7) = \prod M(2,3,5)$$




(a) Active-high decoder with OR gate.

 

(b) Active-low decoder with NAND gate.

 

(c) Active-high decoder with NOR gate.

 


(d) Active-low decoder with AND gate.

# SUMMARY


---

## Encoders

 

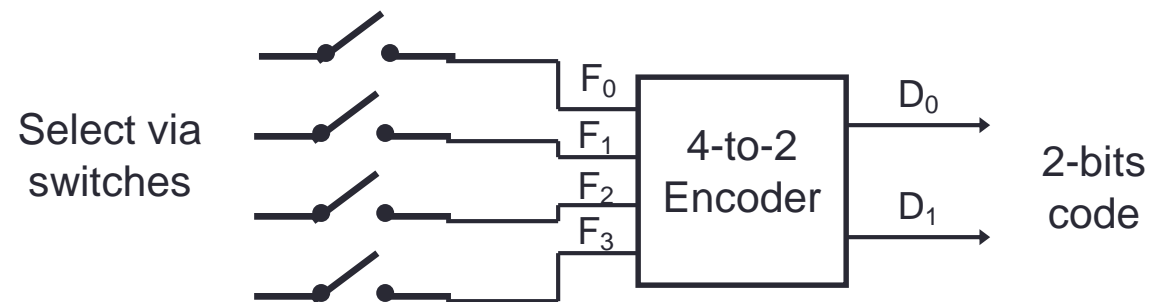
### 3. Encoders (1/4)

- **Encoding** is the converse of decoding.
- Given a set of input lines, of which exactly one is high and the rest are low, the **encoder** provides a code that corresponds to that high input line.
- Contains  $2^n$  (or fewer) input lines and  $n$  output lines.
- Implemented with OR gates.
- Example:






# Encoding – the inefficient way

 


# Encoding – the better way

 

### 3. Encoders (2/4)



- Truth table:
- With K-map, we obtain:
  - $D_1 = F_2 + F_3$
  - $D_0 = F_1 + F_3$

- Circuit:

 

Simple 4-to-2 encoder

$F_0$	$F_1$	$F_2$	$F_3$	$D_1$	$D_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1
0	0	0	0	X	X
0	0	1	1	X	X
0	1	0	1	X	X
0	1	1	0	X	X
0	1	1	1	X	X
1	0	0	1	X	X
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

  


### 3. Encoders (3/4)

- Example: 8-to-3 encoder.
  - At any one time, only one input line of an encoder has a value of 1 (high), the rest are zeroes (low).

Inputs								Outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

### 3. Encoders (4/4)

- Example: 8-to-3 encoder.

 

An 8-to-3 encoder

- Exercise:** Can you design a  $2^n$ -to- $n$  encoder without using K-map?


### 3. Priority Encoders (1/2)

- A **priority encoder** is one with priority
  - To allow for more than one input line to carry a 1.
  - If two or more inputs are equal to 1, the input with the highest priority takes precedence.
  - If all inputs are 0, this input combination is considered invalid.
- Example of a **4-to-2 priority encoder**:

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$f$	$g$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

### 3. Priority Encoders (2/2)

- Understanding “compact” function table



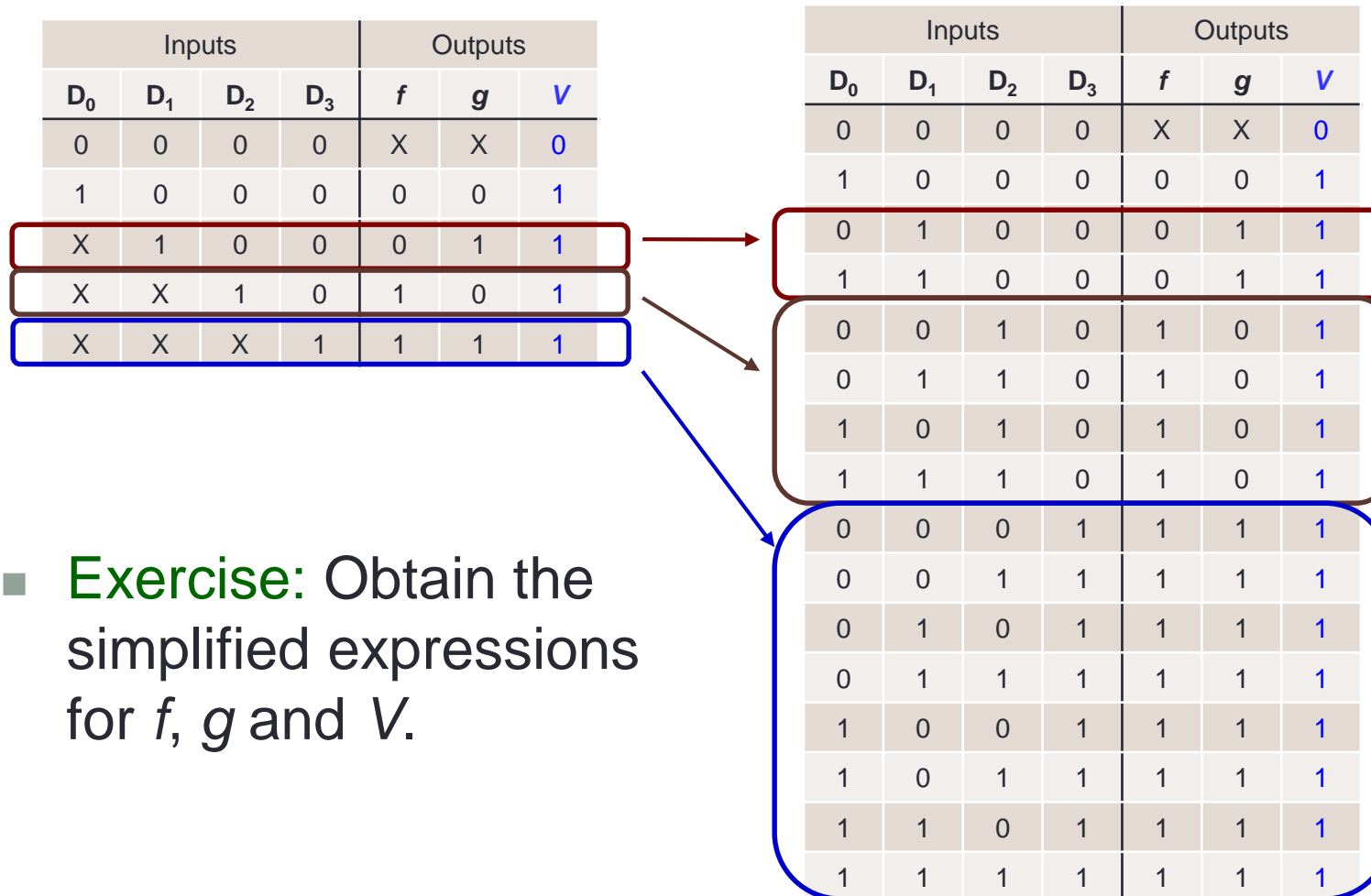


- Exercise:** Obtain the simplified expressions for  $f$ ,  $g$  and  $V$ .

Hi Prof, please go through priority encoder and how to map out the expression using kmap. Slide 34 lect 18.

- **Exercise:** Obtain the simplified expressions for  $f$ ,  $g$  and  $V$ .

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$f$	$g$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
0	1	0	0	0	1	1
1	1	0	0	0	1	1
0	0	1	0	1	0	1
0	1	1	0	1	0	1
1	0	1	0	1	0	1
1	1	1	0	1	0	1
0	0	0	1	1	1	1
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

   





# SUMMARY

---


## Multiplexers

 

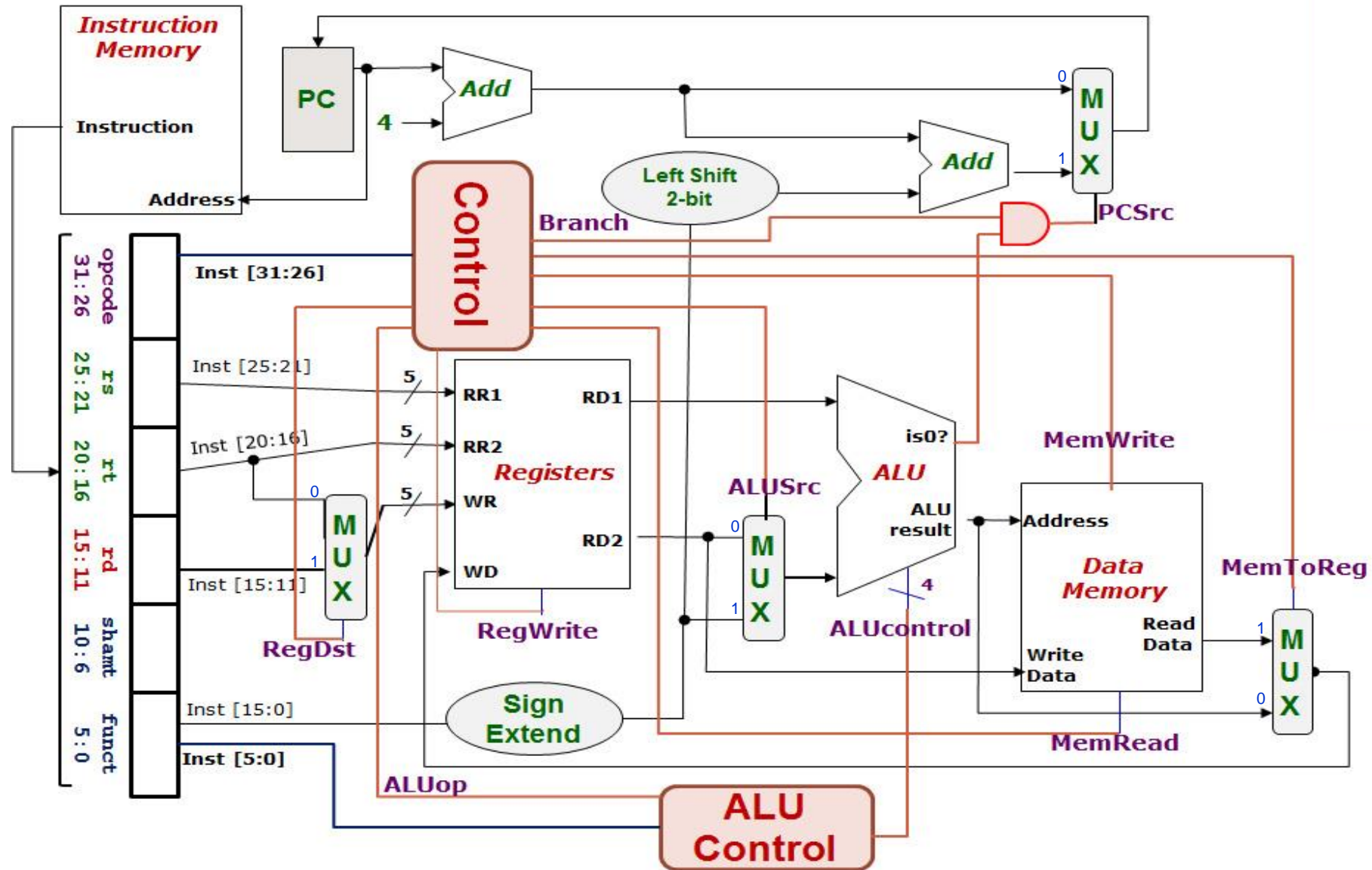

# Multiplexers and Demultiplexers


- An application:

 

- Helps share a *single communication line* among a number of devices.
- At any time, only one source and one destination can use the communication line.
 
## 5. Multiplexers (1/4)

- A **multiplexer** is a device that has
  - A number of input lines
  - A number of selection lines
  - One output line
- It steers one of  $2^n$  inputs to a single output line, using  $n$  selection lines. Also known as a ***data selector***.





## 5. Multiplexers (2/4)

- Truth table for a 4-to-1 multiplexer:

$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
$d_0$	$d_1$	$d_2$	$d_3$	0	0	$d_0$
$d_0$	$d_1$	$d_2$	$d_3$	0	1	$d_1$
$d_0$	$d_1$	$d_2$	$d_3$	1	0	$d_2$
$d_0$	$d_1$	$d_2$	$d_3$	1	1	$d_3$

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

  

## 5. Multiplexers (3/4)

- Output of multiplexer is

“sum of the (product of *data lines* and *selection lines*)”

- Example: Output of a 4-to-1 multiplexer is:

$$Y = I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

*Note:*

Expressing

$$I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$



in minterms notation, it is equal to

$$I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3$$

This is useful later (eg: slide 45).

  
## 5. Multiplexers (4/4)

- A  $2^n$ -to-1-line multiplexer, or simply  $2^n:1$  MUX, is made from an  $n:2^n$  decoder by adding to it  $2^n$  input lines, one to each AND gate.
- A **4:1 multiplexer circuit:**



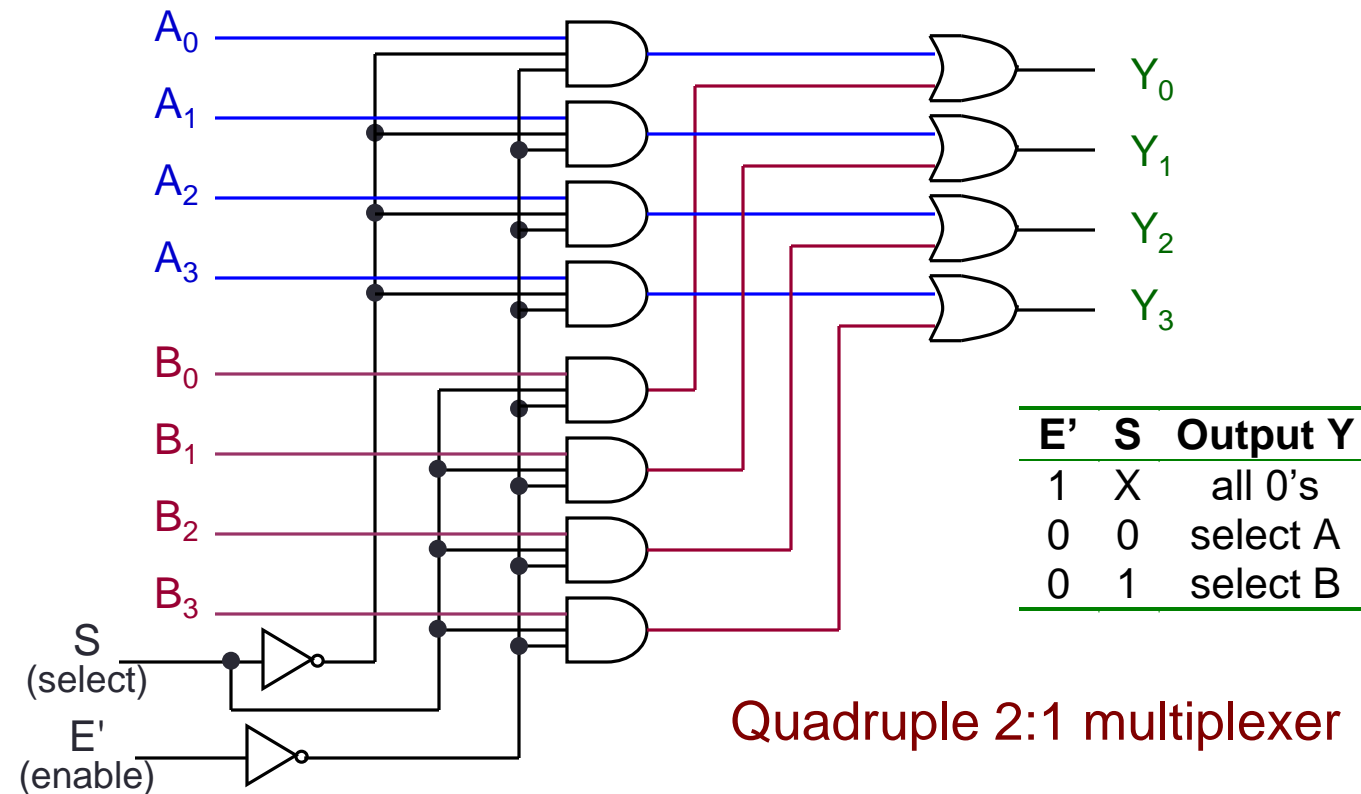
## 5. Multiplexer IC Package

- Some IC packages have a few multiplexers in each package (chip). The selection and enable inputs are common to all multiplexers within the package.





## 5. Standard MSI Multiplexer (1/2)

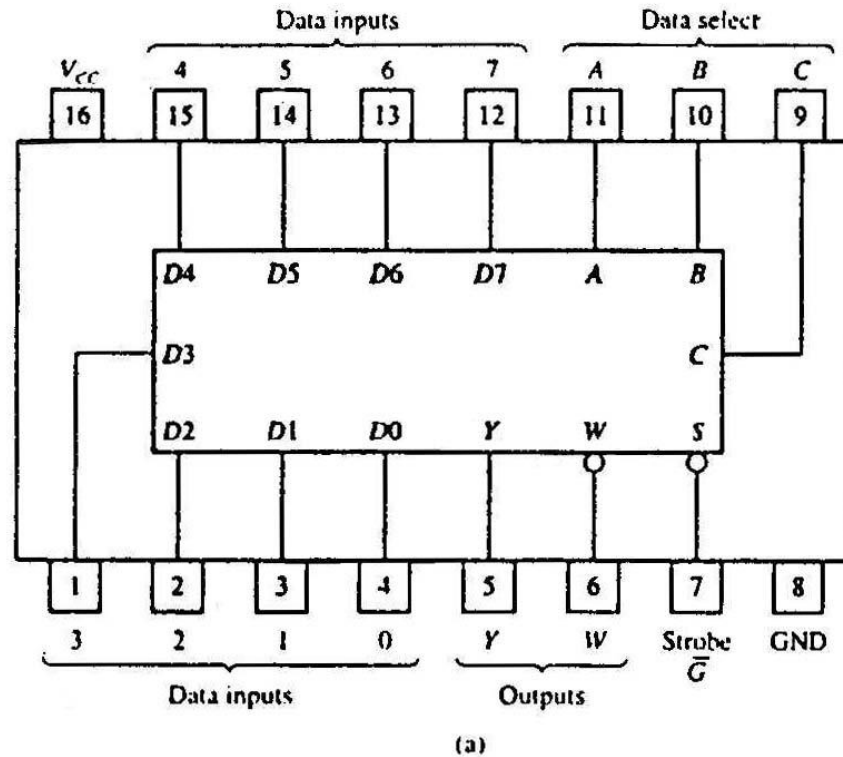


INPUTS				OUTPUTS	
SELECT			STROBE $\overline{G}$	Y	W
C	B	A			
X	X	X	H	L	H
L	L	L	L	D0	$\overline{D0}$
L	L	H	L	D1	$\overline{D1}$
L	H	L	L	D2	$\overline{D2}$
L	H	H	L	D3	$\overline{D3}$
H	L	L	L	D4	$\overline{D4}$
H	L	H	L	D5	$\overline{D5}$
H	H	L	L	D6	$\overline{D6}$
H	H	H	L	D7	$\overline{D7}$

(b)

**74151A 8-to-1 multiplexer.** (a) Package configuration. (b) Function table.

## 5. Standard MSI Multiplexer (2/2)

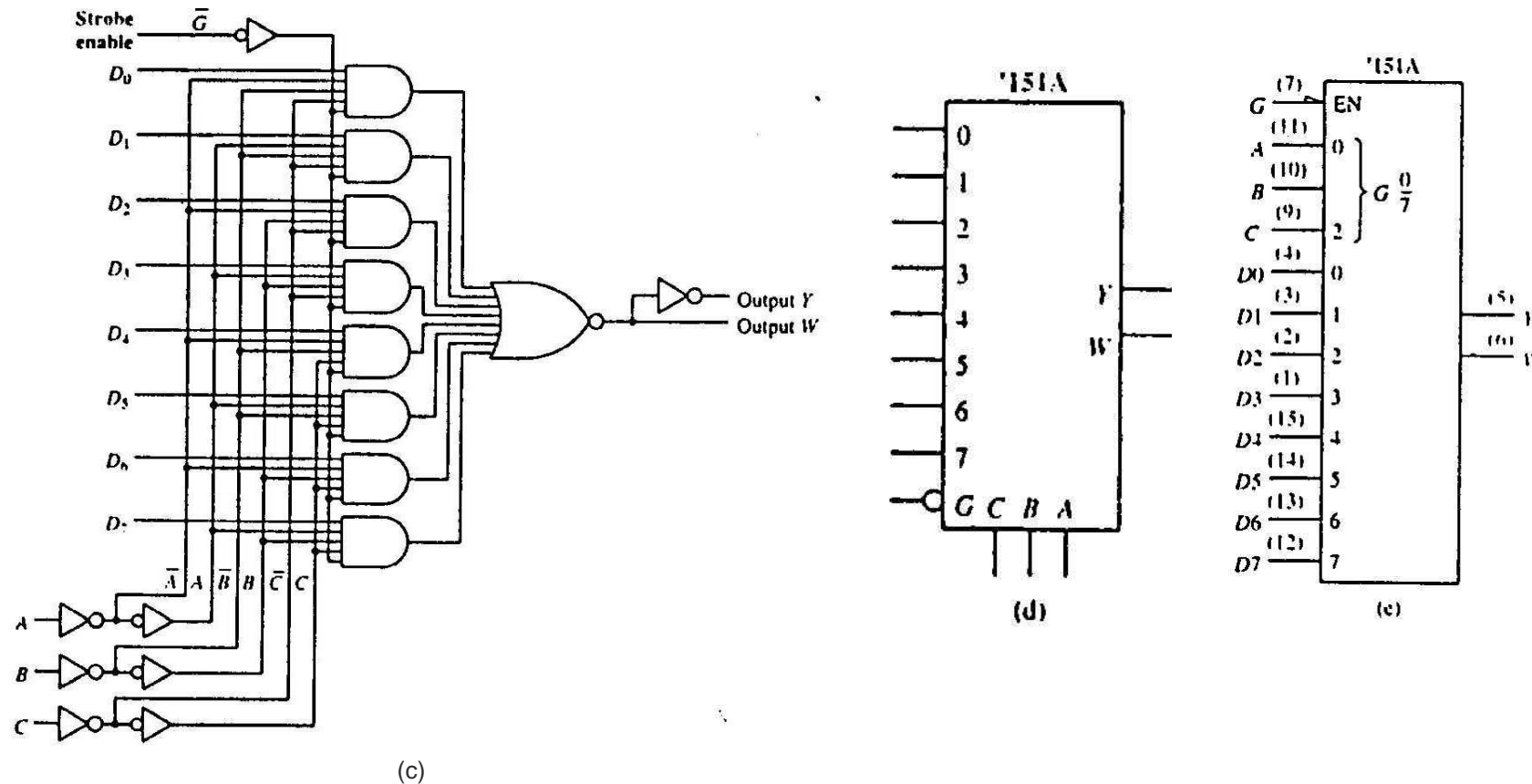

**74151A 8-to-1 multiplexer.** (c) Logic diagram. (d) Generic logic symbol.  
(e) IEEE standard logic symbol.

Source: *The TTL Data Book Volume 2. Texas Instruments Inc., 1985.*

## 5. Multiplexers: Implementing Functions (1/3)

- Boolean functions can be implemented using multiplexers.
- A  $2^n$ -to-1 multiplexer can implement a Boolean function of  $n$  input variables, as follows:

1. Express in sum-of-minterms form.


Example:

$$\begin{aligned} F(A,B,C) &= A' \cdot B' \cdot C + A' \cdot B \cdot C + A \cdot B' \cdot C + A \cdot B \cdot C' \\ &= \Sigma m(1,3,5,6) \end{aligned}$$

2. Connect  $n$  variables to the  $n$  selection lines.
3. Put a '1' on a data line if it is a minterm of the function, or '0' otherwise.

## 5. Multiplexers: Implementing Functions (2/3)

■  $F(A,B,C) = \Sigma m(1,3,5,6)$

 

This method works because:

$$\text{Output} = I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3 \\ + I_4 \cdot m_4 + I_5 \cdot m_5 + I_6 \cdot m_6 + I_7 \cdot m_7$$

Supplying '1' to  $I_1, I_3, I_5, I_6$ , and '0' to the rest:

$$\text{Output} = m_1 + m_3 + m_5 + m_6$$

*From slide 34 (4:1 mux)*

Expressing

$$I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$

in minterms notation, it is equal to

$$I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3$$

## 5. Multiplexers: Implementing Functions (3/3)

- Example: Use a 74151A to implement  

$$f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$$


$i$	$C$	$B$	$A$	$Y$
	$x_1$	$x_2$	$x_3$	$f$
0	0	0	0	1 $D_0 = 1$
1	0	0	1	0 $D_1 = 0$
2	0	1	0	1 $D_2 = 1$
3	0	1	1	1 $D_3 = 1$
4	1	0	0	0 $D_4 = 0$
5	1	0	1	1 $D_5 = 1$
6	1	1	0	0 $D_6 = 0$
7	1	1	1	0 $D_7 = 0$

(a)

Realization of  $f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$ .

(a) Truth table.

(b) Implementation with 74151A.

 



## 5. Using Smaller Multiplexers (1/6)

- Earlier, we saw how a  $2^n$ -to-1 multiplexer can be used to implement a Boolean function of  $n$  (input) variables.
- However, we can use a single smaller  $2^{(n-1)}$ -to-1 multiplexer to implement a Boolean function of  $n$  (input) variables.
- Example: The function
$$F(A,B,C) = \Sigma m(1,3,5,6)$$
can be implemented using a 4-to-1 multiplexer (rather than an 8-to-1 multiplexer).
  
## 5. Using Smaller Multiplexers (2/6)

- Let's look at this example:

$$F(A,B,C) = \sum m(0,1,3,6) = A' \cdot B' \cdot C' + A' \cdot B' \cdot C + A' \cdot B \cdot C + A \cdot B \cdot C'$$



- Note: Two of the variables, **A** and **B**, are applied as selection lines of the multiplexer, while the inputs of the multiplexer contain **1**, **C**, **0** and **C'**.

## 5. Using Smaller Multiplexers (3/6)

### ■ Procedure

1. Express Boolean function in sum-of-minterms form.

Example:  $F(A,B,C) = \sum m(0,1,3,6)$

2. Reserve one variable (in our example, we take the least significant one) for input lines of multiplexer, and use the rest for selection lines.


Example:  $C$  is for input lines;  $A$  and  $B$  for selection lines.



## 5. Using Smaller Multiplexers (4/6)

3. Draw the truth table for function, by grouping inputs by selection line values, then determine multiplexer inputs by comparing input line (**C**) and function (**F**) for corresponding selection line values.


A	B	C	F	MUX input
0	0	0	1	<b>1</b>
0	0	1	1	
0	1	0	0	<b>C</b>
0	1	1	1	
1	0	0	0	<b>0</b>
1	0	1	0	
1	1	0	1	<b>C'</b>
1	1	1	0	

 

## 5. Using Smaller Multiplexers (5/6)

- Alternative: What if we use **A** for input lines, and **B**, **C** for selector lines?

A	B	C	F	Mux Input
0	0	0	1	1
0	0	1	1	
0	1	0	0	C
0	1	1	1	
1	0	0	0	0
1	0	1	0	
1	1	0	1	C'
1	1	1	0	

 

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$A'$  (when  $BC = 00$ )  
 $A'$  (when  $BC = 01$ )  
 $A$  (when  $BC = 10$ )  
 $A'$  (when  $BC = 11$ )


## 5. Using Smaller Multiplexers (6/6)

- Example: Implement the function below with 74151A:

$$f(x_1, x_2, x_3, x_4) = \Sigma m(0, 1, 2, 3, 4, 9, 13, 14, 15)$$

	C	B	A				Y
i	X <sub>1</sub>	X <sub>2</sub>	X <sub>3</sub>	X <sub>4</sub>	f	f	
0	0	0	0	0	1		
	0	0	0	1	1	1	D <sub>0</sub> = 1
1	0	0	1	0	1		
	0	0	1	1	1	1	D <sub>1</sub> = 1
2	0	1	0	0	1		
	0	1	0	1	0	$\bar{X}_4$	D <sub>2</sub> = $\bar{X}_4$
3	0	1	1	0	0		
	0	1	1	1	0	0	D <sub>3</sub> = 0
4	1	0	0	0	0		
	1	0	0	1	1	X <sub>4</sub>	D <sub>4</sub> = X <sub>4</sub>
5	1	0	1	0	0		
	1	0	1	1	0	0	D <sub>5</sub> = 0
6	1	1	0	0	0		
	1	1	0	1	1	X <sub>4</sub>	D <sub>6</sub> = X <sub>4</sub>
7	1	1	1	0	1		
	1	1	1	1	1	1	D <sub>7</sub> = 1

(a)

 


(b)
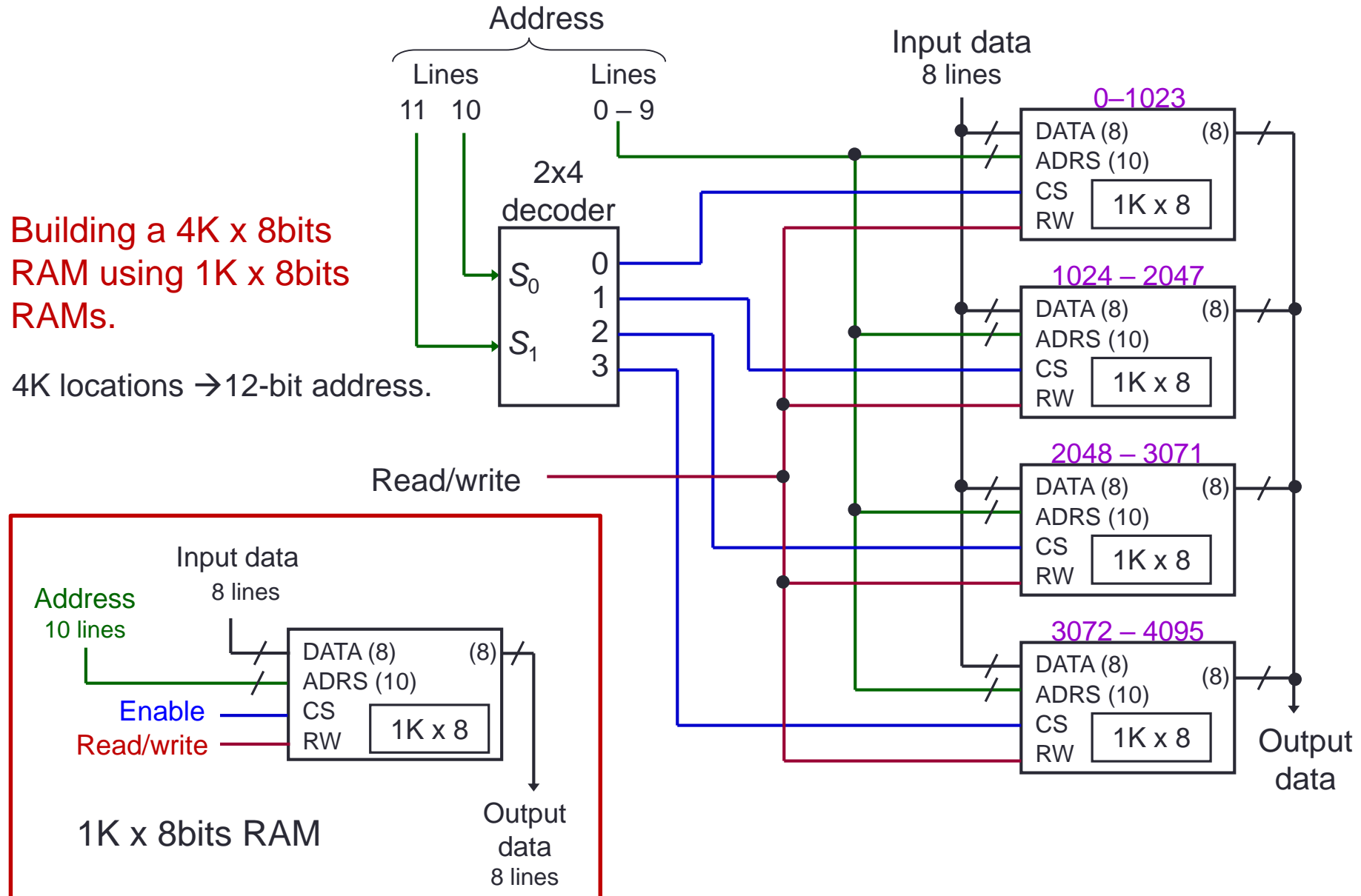
# Peeking Ahead

Building a 4K x 8bits  
RAM using 1K x 8bits  
RAMs.


4K locations  $\rightarrow$  12-bit address.


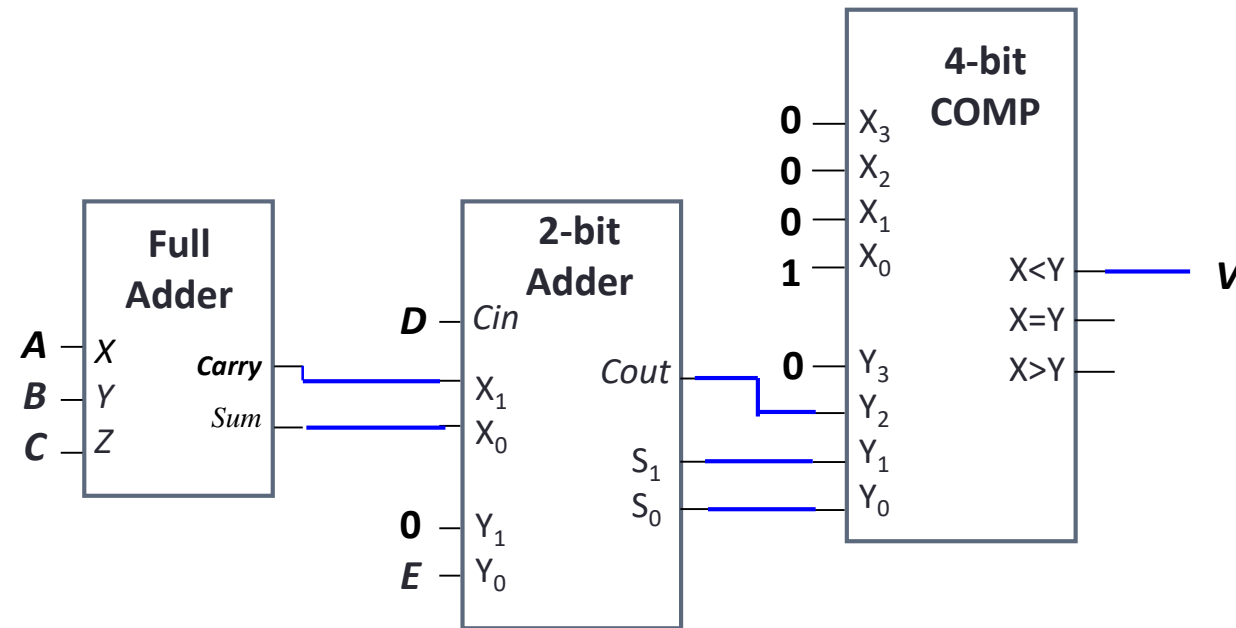
# QNA QUERIES (PAST SEMESTER'S)

---


For tutorial 7 q1 why is the 2nd input 0 and E why it cannot be D and E?



Can you go through tutorial 7 q2?

Q2(a)  $EFGH = (ABCD + 1)/2$


A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	1
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	0
1	0	0	1	0	1	0	1
1	0	1	0	0	1	0	1
1	0	1	1	0	1	1	0
1	1	0	0	0	1	1	0
1	1	0	1	0	1	1	1
1	1	1	0	0	1	1	1
1	1	1	1	1	0	0	0

 

Can you go through tutorial 7 q2?

Q2(a)  $EFGH = (ABCD+1)/2$

A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	1
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	0
1	0	0	1	0	1	0	1
1	0	1	0	0	1	0	1
1	0	1	1	0	1	1	0
1	1	0	0	0	1	1	0
1	1	0	1	0	1	1	1
1	1	1	0	0	1	1	1
1	1	1	1	1	0	0	0

 




Can you go through tutorial 7 q2?

Q2(b) 4221-to-8421 decimal code converter

<i>P</i>	<i>Q</i>	<i>R</i>	<i>S</i>	<i>W</i>	<i>X</i>	<i>Y</i>	<i>Z</i>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	1	0	0	1	0	0
1	0	0	1	0	1	0	1
1	1	0	0	0	1	1	0
1	1	0	1	0	1	1	1
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	1

 

# PAST YEARS' QUESTIONS

---

MSI Components

## Past years' exam questions

- AY2016/17 Sem2 Q2
- AY2017/18 Sem2 Q3(a)(b)(c)
- AY2018/19 Sem2 Q5(c)
- AY2019/20 Sem2 Q5(a)(b)

## Assumption

- Logical constants 0 and 1 are available, but not complemented literals.


# AY2016/17 Sem2 Q2(a)

2. [10 marks]

 a. Given the following Boolean function:

$$F(A,B,C,D) = \sum m(1, 4, 5, 6, 7, 13)$$

You are to implement  $F$  using a single **2-bit magnitude comparator** with no additional logic gates. Note that complemented literals are not available. [5 marks]



Observe that

$$F = AC < BD$$

Other answers possible.


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

# AY2016/17 Sem2 Q2(b)

 b. Given the following Boolean function:

$$G(A,B,C,D) = \sum m(2, 11)$$

You are to implement  $G$  using a single **2×4 decoder** with one-enable and active high outputs, and one 2-input exclusive-OR gate. Note that complemented literals are not available. [5 marks]



Observe that


$$\begin{aligned} G(A,B,C,D) &= \sum m(2, 11) \\ &= A' \cdot B' \cdot C \cdot D' + A \cdot B' \cdot C \cdot D \\ &= C \cdot ((A' \cdot D' + A \cdot D) \cdot B') \\ &= C \cdot ((A \oplus D)' \cdot B') \end{aligned}$$

# AY2017/18 Sem2 Q3(a)

3. [20 marks]

(a) Given the following circuit, what is  $F$ ?

[4 marks]

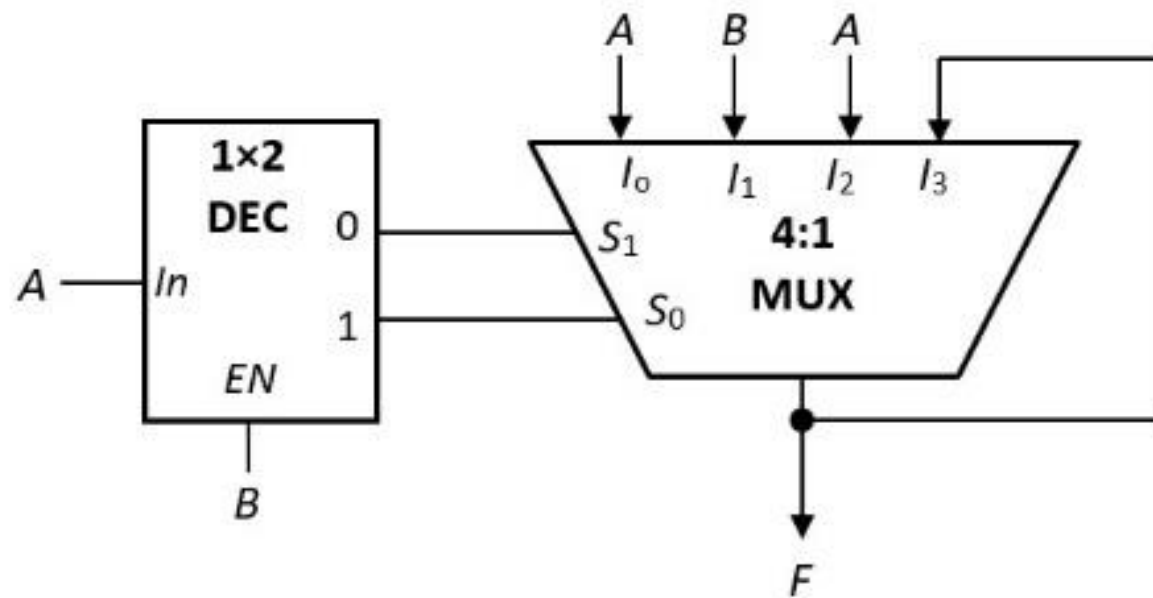


$A$	$B$	$F$
0	0	0
0	1	0
1	0	1
1	1	1

$$F = A$$

# AY2017/18 Sem2 Q3(b)

 
- (b) Given  $G(A,B,C,D) = \prod M(1, 2, 6, 8, 9, 11, 13)$ , implement  $G$  using a single 8:1 multiplexer without any additional logic gates. Complemented literals are not available. [4 marks]



A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

# AY2017/18 Sem2 Q3(c)

 - (c) Given  $H(A,B,C,D) = \sum m(12, 13)$ , implement  $H$  using a single 2×4 active high output decoder with 1-enable, without any additional logic gates. Complemented literals are not available. [4 marks]



$$\begin{aligned}
 H(A,B,C,D) &= \sum m(12, 13) \\
 &= A \cdot B \cdot C' \cdot D' + A \cdot B \cdot C' \cdot D \\
 &= A \cdot (B \cdot C' \cdot D' + B \cdot C' \cdot D) \\
 &= A \cdot (B \cdot C')
 \end{aligned}$$


Other alternative answers possible.



# AY2018/19 Sem2 Q5(c)

 - (c) Assuming that the 8-bit input ABCDEFGH is an unsigned binary number. Let  $Q(A,B,C,D,E,F,G,H)$  be a Boolean function that returns 1 if ABCDEFGH is a multiple of 17 (eg: 0, 17, 34, 51, etc.), or returns 0 otherwise.

Given a **parallel adder**, a **magnitude comparator**, a **decoder**, an **encoder**, and a **demultiplexer**, implement  $Q$  using only ONE of these devices, without any additional logic gates. Your device should be the smallest possible (for example, if an 8-bit parallel adder is sufficient, you should not use a 16-bit parallel adder). [4 marks]



$$\begin{aligned}
 0_{10} &= 0000 \ 0000_2 \\
 17_{10} &= 0001 \ 0001_2 \\
 34_{10} &= 0010 \ 0010_2 \\
 51_{10} &= 0011 \ 0011_2 \\
 68_{10} &= 0100 \ 0100_2 \\
 85_{10} &= 0101 \ 0101_2 \\
 &\vdots \\
 255_{10} &= 1111 \ 1111_2
 \end{aligned}$$


# AY2019/20 Sem2 Q5(a)

## 5. [12 marks]

For the parts below, you are to assume that logical constants 0 and 1 are available but complemented literals are not available.

- (a) A device **NonZero** takes in a 3-bit unsigned number  $ABC$ . Its output,  $N$ , is 0 if the value represented by  $ABC$  is 0, or 1 if the value represented by  $ABC$  is not zero.
- (i) Write the simplified SOP expression for  $N$ . [2 marks]
- (ii) Implement  $N$  using the following single 2x4 decoder with zero-enable and negated outputs, with no other logic gates and devices. [4 marks]


A	B	C	N
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

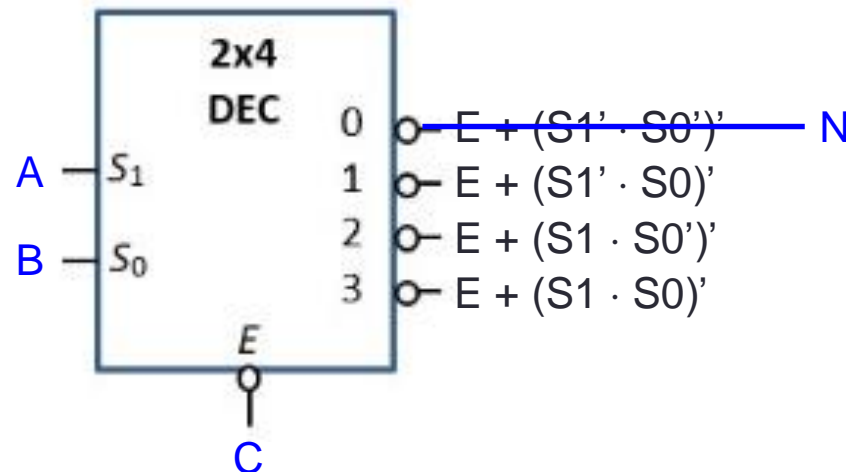

$$N = A + B + C$$

# AY2019/20 Sem2 Q5(b)

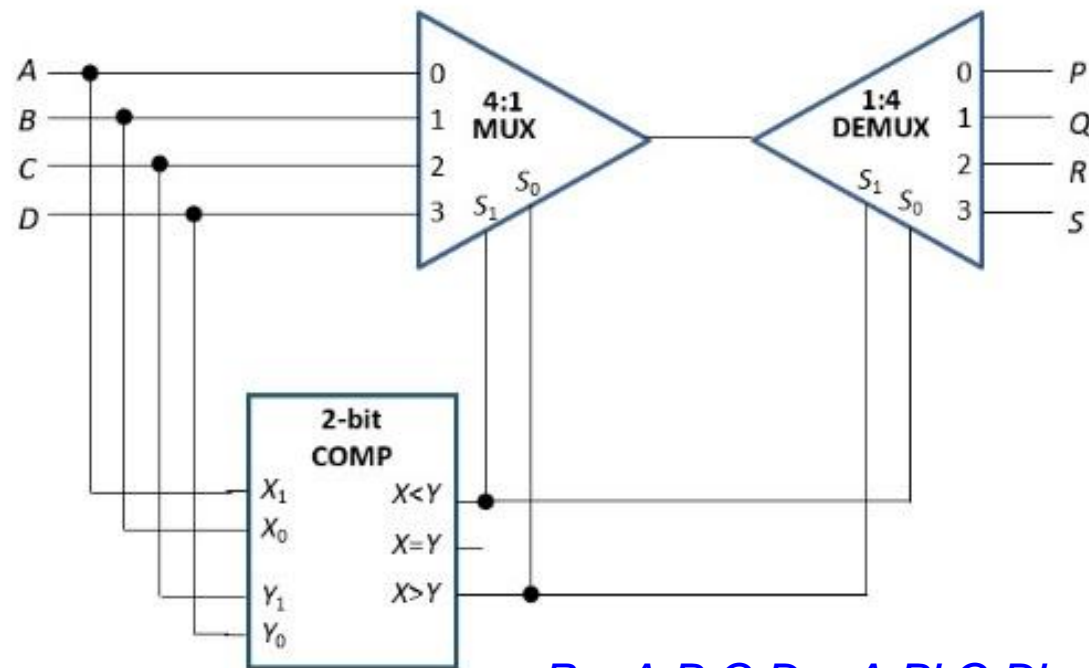- (b) The circuit below uses a 2-bit magnitude comparator, a 4:1 multiplexer and a 1:4 demultiplexer. Inputs are  $A, B, C, D$  and outputs are  $P, Q, R, S$ . Write the simplified SOP expressions for  $P, Q$  and  $R$ . [6 marks]



$$P = A \cdot B \cdot C \cdot D + A \cdot B' \cdot C \cdot D'$$

$$Q = A' \cdot C + B' \cdot C \cdot D$$

$$R = B \cdot C' \cdot D' + A \cdot B \cdot C' + A \cdot B \cdot D'$$

$AB$	$CD$	$AB < CD$	$AB > CD$	(MUX) $S_1 S_0$	(DEMUX) $S_1 S_0$	$PQRS$	$PQRS$
00	00	0	0	00	00	A000	0000
00	01	1	0	10	01	0C00	0000
00	10	1	0	10	01	0C00	0100
00	11	1	0	10	01	0C00	0100
01	00	0	1	01	10	00B0	0010
01	01	0	0	00	00	A000	0000
01	10	1	0	10	01	0C00	0100
01	11	1	0	10	01	0C00	0100
10	00	0	1	01	10	00B0	0000
10	01	0	1	01	10	00B0	0000
10	10	0	0	00	00	A000	1000
10	11	1	0	10	01	0C00	0100
11	00	0	1	01	10	00B0	0010
11	01	0	1	01	10	00B0	0010
11	10	0	1	01	10	00B0	0010
11	11	0	0	00	00	A000	1000

# QUIZ

---


## 21. MSI Components Quiz

# Question 1
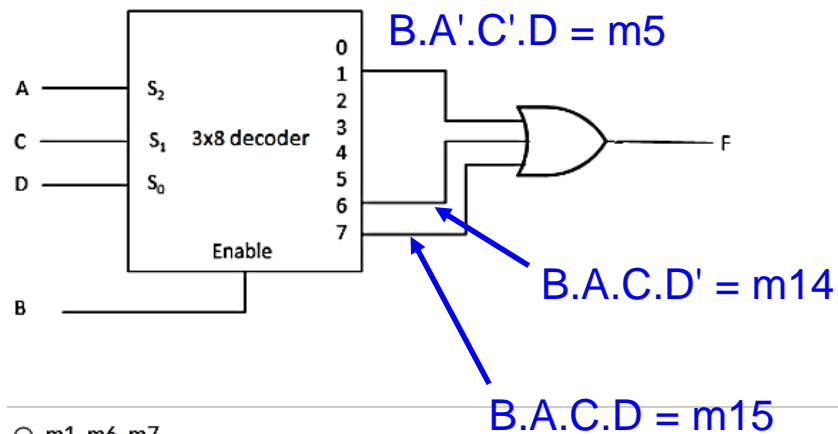
## Question 1

1 pts

The following circuit implements a function  $F(A, B, C, D)$ . What minterms does it produce? This decoder has an active high Enable line, and active high outputs.



- ☐ m1, m6, m7  
☐ m3, m5, m15  
☒ m5, m14, m15  
☐ m3, m13, m15


A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

# Question 2
 
## Question 2

1 pts

We see a circuit for  $G(A, B, C)$ . What minterms does this circuit produce? Note that this is a common way of drawing multiplexors, instead of the rectangles used in the lectures.



BC = 00

BC = 01

BC = 10

BC = 11

A	B	C	G
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

☒ m2, m3, m5, m7

☐ m0, m2, m4, m7

☐ m1, m2, m6, m7

☐ m0, m2, m5, m7

# ~~NEXT WEEK~~ THIS THURSDAY

---

## Sequential Circuits

Online recitation on 27 March 2025, Thursday, 4pm

- Zoom link on Canvas > Zoom

Past years' exam questions:

- AY2015/16 Sem1 Q7
- AY2020/21 Sem2 Q12

End of File