

# CS2100

## Recitation 10

---

### Sequential Circuits

31 March 2025

(Make-up on 27 March 2025)


Aaron Tan

# Contents

- Latches
- Flip-flops
- Analysis of Sequential Circuits
- Design of Sequential Circuits
- ~~■ Quizzes~~
- Selected Past Years' Exam Questions
  - AY2015/16 Sem1 Q7
  - AY2020/21 Sem2 Q12

 
# 1. Introduction


- Two classes of logic circuits
  - Combinational
  - Sequential
- **Combinational Circuit**
  - Each output depends entirely on the immediate (present) inputs.



2 weeks ago...

 - **Sequential Circuit**
  - Each output depends on both present inputs and state.



 

# SUMMARY


---

## Latches


## 3.1 S-R Latch (2/3)

**Key:** When tracing a latch/flip-flop, do it 3 rounds.

- Active-high input S-R latch:

 

- Block diagram:


 


- Characteristic table:

S	R	Q(t+1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	indeterminate	
  
## 3.1 Active-Low S-R Latch

- (You may skip this slide.)
- What we have seen is **active-high input** S-R latch.
- There are **active-low input** S-R latches, where NAND gates are used instead. See diagram on the left below.




- In this case,
  - when  $R=0$  and  $S=1$ , the latch is reset (i.e. Q becomes 0)
  - when  $R=1$  and  $S=0$ , the latch is set (i.e. Q becomes 1)
  - when  $S=R=1$ , it is a no-change command.
  - when  $S=R=0$ , it is an invalid command.
- Sometimes, we use the alternative gate diagram for the NAND gate. See diagram on the right above. (This appears in more complex latches/flip-flops in the later slides.)

(Sometimes, the inputs are labelled as  $S'$  and  $R'$ .)


# 3.1 Active-High vs Active-Low S-R Latch

**(Active-high) S-R latch**

 

S	R	$Q(t+1)$	Command
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Invalid

**Active-low S-R latch**

 


S	R	$Q(t+1)$	Command
1	1	$Q(t)$	No change
1	0	0	Reset
0	1	1	Set
0	0	?	Invalid


 
## 3.1 Gated S-R Latch

- S-R latch + *enable input* ( $EN$ ) and 2 NAND gates  
→ a **gated S-R latch**.




- Outputs change (if necessary) only when  $EN$  is high.
- Characteristic table:

$EN$	$S$	$R$	$Q(t+1)$	Command
1	0	0	$Q(t)$	No change
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	?	Invalid
0	X	X	$Q(t)$	
 
## 3.2 Gated $D$ Latch (1/2)

- Make input  $R$  equal to  $S' \rightarrow$  **gated  $D$  latch**.
- $D$  latch eliminates the undesirable condition of invalid state in the  $S$ - $R$  latch.



- Characteristic table:

$EN$	$D$	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change


# SUMMARY

---

## Flip-Flops

 
## 4. Flip-flops (1/2)

- Flip-flops are synchronous bistable devices.
- Output changes state at a specified point on a triggering input called the **clock**.
- Change state either at the positive (rising) edge, or at the negative (falling) edge of the clock signal.


 
## 4.1 S-R Flip-flop

- **S-R flip-flop**: On the triggering edge of the clock pulse,
  - $R = \text{HIGH}$  and  $S = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
  - $S = \text{HIGH}$  and  $R = \text{LOW} \rightarrow Q$  becomes HIGH (SET state)
  - Both  $R$  and  $S$  are LOW  $\rightarrow$  No change in output  $Q$
  - Both  $R$  and  $S$  are HIGH  $\rightarrow$  Invalid!
- **Characteristic table** of positive edge-triggered S-R flip-flop:




S	R	CLK	$Q(t+1)$	Comments
0	0	X	$Q(t)$	No change
0	1	$\uparrow$	0	Reset
1	0	$\uparrow$	1	Set
1	1	$\uparrow$	?	Invalid

X = irrelevant ("don't care")

$\uparrow$  = clock transition LOW to HIGH
 
## 4.2 *D* Flip-flop (1/2)

- *D* flip-flop: Single input *D* (data). On the triggering edge of the clock pulse,
  - $D = \text{HIGH} \rightarrow Q$  becomes HIGH (SET state)
  - $D = \text{LOW} \rightarrow Q$  becomes LOW (RESET state)
- Hence, *Q* “follows” *D* at the clock edge.
- Convert *S-R* flip-flop into a *D* flip-flop: add an inverter.




A positive edge-triggered *D* flip-flop formed with an *S-R* flip-flop.

<i>D</i>	<i>CLK</i>	<i>Q</i> ( <i>t</i> +1)	Comments
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH

## 4.3 J-K Flip-flop (2/2)

- J-K flip-flop circuit:

 

- Characteristic table:


J	K	CLK	$Q(t+1)$	Comments
0	0	↑	$Q(t)$	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	$Q(t)'$	Toggle

$$Q(t+1) = J \cdot Q' + K' \cdot Q$$

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0
 
## 4.4 $T$ Flip-flop

- $T$  flip-flop: Single input version of the  $J$ - $K$  flip-flop, formed by tying both inputs together.



- Characteristic table:

$T$	$CLK$	$Q(t+1)$	Comments
0	$\uparrow$	$Q(t)$	No change
1	$\uparrow$	$Q(t)'$	Toggle

$Q$	$T$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = T \cdot Q' + T' \cdot Q$$




## 5. Asynchronous Inputs (1/2)

- $S$ - $R$ ,  $D$  and  $J$ - $K$  inputs are **synchronous inputs**, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock; example: *preset* ( $PRE$ ) and *clear* ( $CLR$ ) [or *direct set* ( $SD$ ) and *direct reset* ( $RD$ )].
- When  $PRE$ =HIGH,  $Q$  is immediately set to HIGH.
- When  $CLR$ =HIGH,  $Q$  is immediately cleared to LOW.
- Flip-flop in normal operation mode when both  $PRE$  and  $CLR$  are LOW.
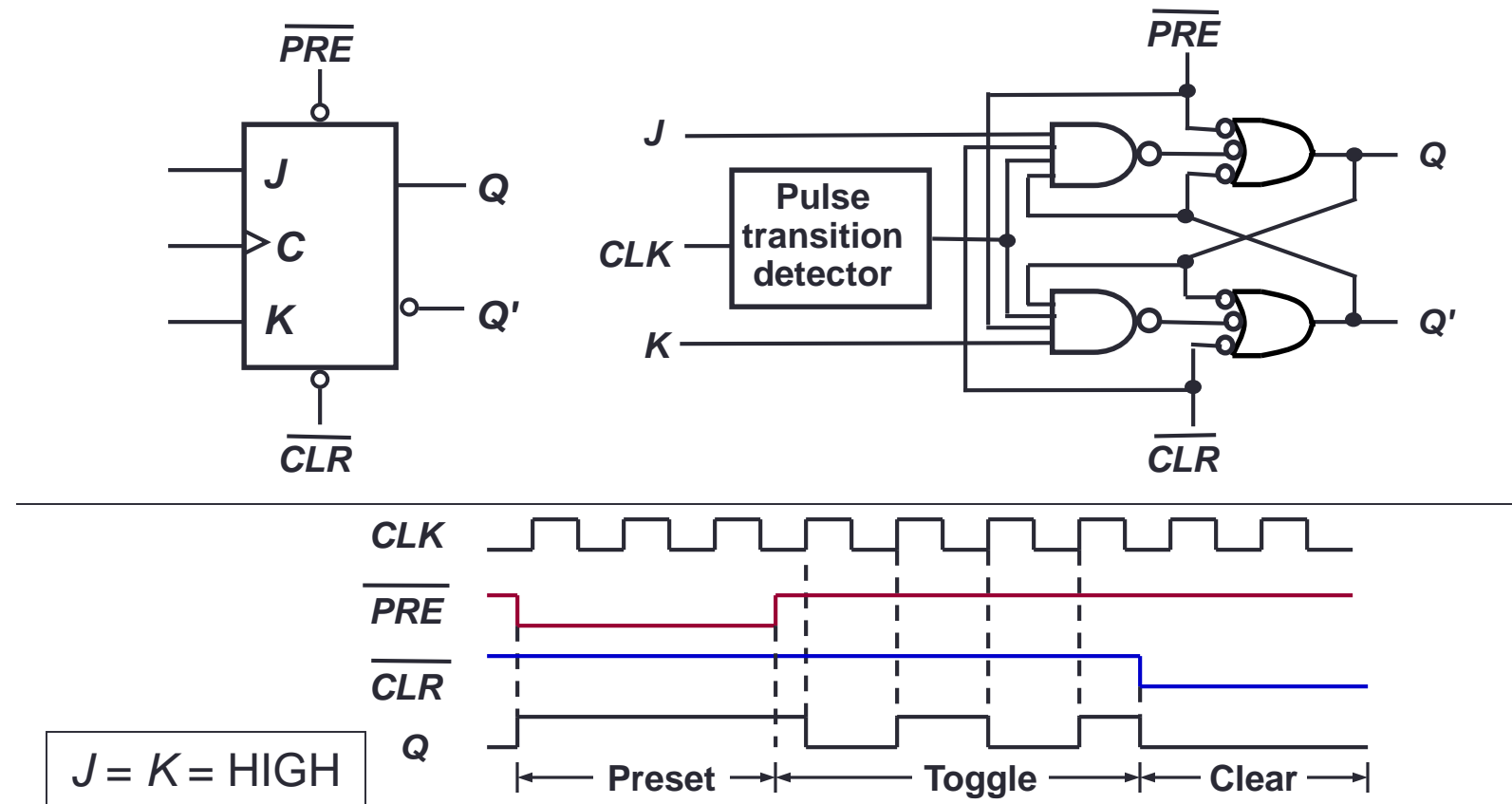
## 5. Asynchronous Inputs (2/2)

- A  $J$ - $K$  flip-flop with active-low PRESET and CLEAR asynchronous inputs.



# COMMON QUESTIONS

---

From previous semester

Q1: How does slide 9 of lect 19 work? Why is it that both R and S are high considered an invalid input?

A: It has been illustrated that when both R and S are high, the output Q and Q' are the same, which violates the definition of a latch/flip-flop.

Q2: Does  $Q(t+1)$ ,  $Q^+$  and  $Q'$  all mean the same thing?


A:  $Q(t)$  and  $Q(t+1)$  mean present state and next state respectively. They can also be referred to simply as Q and  $Q^+$  respectively. So,  $Q = Q(t)$ , and  $Q^+ = Q(t+1)$ .

$Q'$  is the complement of Q. Therefore,  $Q'$  is not the same as Q (in fact, it is the negation/opposite of Q), nor is it the same as  $Q^+$  (it has no relationship to  $Q^+$ ).


Q3: L19 slide 10, the outputs are redirected as inputs, and to get outputs we need inputs first. How does the whole thing work as it seems like a never-ending cycle.

A: If there isn't a clock, will be a "never-ending cycle". The clock provides synchronisation. The flip flop acts only when it is activated (by the rising edge or falling edge of the clock).

 Q4: Why is there a circle at Q' output on the flip flop?




Positive edge-triggered flip-flops

 

Negative edge-triggered flip-flops

A: Just a labelling convention, to remind users that the output (Q') is the negation of Q.

 Q5: What do  $Q$  and  $Q'$  represent on the flip flop?





Positive edge-triggered flip-flops

A:  $Q$  is the state of the flip-flop and  $Q'$  is the negation of  $Q$ .

A flip-flop is a one-bit memory unit; when it stores a 0 it is said to be in the reset state; when it stores a 1 it is in the set state. The  $Q$  output of a flip-flop determines the state it is in.
  
# Analysis

Uses flip-flop  
characteristic  
tables.



## State diagram

# Design

Uses flip-flop  
excitation  
tables.

Just for illustration. The state diagram here does not correspond to the logic circuit.

# SUMMARY

---

## Analysis of Sequential Circuits



## 6.1 Flip-flop Characteristic Tables

- Each type of flip-flop has its own behaviour, shown by its **characteristic table**.

$J$	$K$	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

$S$	$R$	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

$D$	$Q(t+1)$
0	0      Reset
1	1      Set

$T$	$Q(t+1)$
0	$Q(t)$ No change
1	$Q(t)'$ Toggle



## 6.2 Analysis: Example #2 (2/3)

$$JA = B$$

$$KA = B \cdot x'$$

$$JB = x'$$

$$KB = A' \cdot x + A \cdot x' = A \oplus x$$

- Fill the **state table** using the above functions, knowing the characteristics of the flip-flops used.

<i>J</i>	<i>K</i>	<i>Q(t+1)</i>	Comments
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q(t)'</i>	Toggle


  

Present state		Input <i>x</i>	Next state		Flip-flop inputs			
<i>A</i>	<i>B</i>		<i>A</i> <sup>+</sup>	<i>B</i> <sup>+</sup>	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

## 6.2 Analysis: Example #2 (3/3)

- Draw the **state diagram** from the state table.

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 

# SUMMARY

---

## Design of Sequential Circuits

## 6.3 Flip-flop Excitation Tables (1/2)

- *Excitation tables*: given the required transition from present state to next state, determine the flip-flop input(s).

$Q$	$Q^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$JK$  Flip-flop

$Q$	$Q^+$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$SR$  Flip-flop

$Q$	$Q^+$	$D$
0	0	0
0	1	1
1	0	0
1	1	1


$D$  Flip-flop

$Q$	$Q^+$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

$T$  Flip-flop
 
## 6.4 Design: Example #1 (1/5)

- Given the following state diagram, design the sequential circuit using *JK* flip-flops.



### Questions:

How many flip-flops are needed?

How many input variable are there?

### Answers:

Two flip-flops.


Let's call them *A* and *B*.

One input variable.

Let's call it *x*.
 
## 6.4 Design: Example #1 (2/5)

- Circuit state/excitation table, using  $JK$  flip-flops.



$Q$	$Q^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$JK$  Flip-flop's  
excitation table.

Present State	Next State	
	$x=0$	$x=1$
$AB$	$A^+B^+$	$A^+B^+$
00	00	01
01	10	01
10	10	11
11	11	00




Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1



## 6.4 Design: Example #1 (3/5)





- Block diagram.

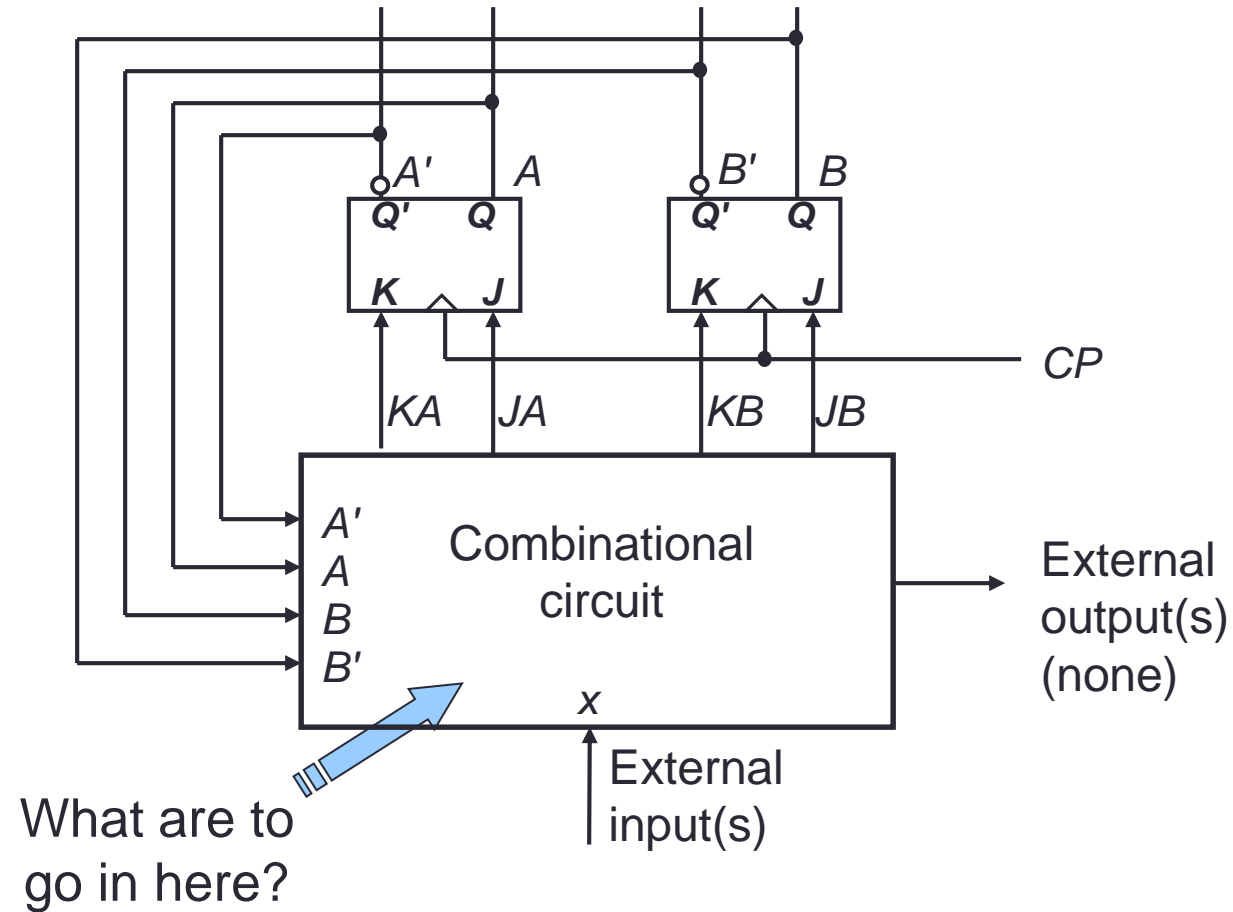

## 6.4 Design: Example #1 (4/5)

- From **state table**, get **flip-flop input functions**.

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

    





## 6.4 Design: Example #3 (2/4)

- From state table, obtain expressions for flip-flop inputs.

		$C$			
		00	01	11	10
$A$	00	X	X	0	0
	01	0	1	1	0
	11	X	X	X	X
	10	X	X	X	0

$SA = B \cdot x$

		$C$			
		00	01	11	10
$A$	00	X	X	X	X
	01	X	0	0	X
	11	X	X	X	X
	10	0	0	0	1

$RA = C \cdot x'$

---

		$C$			
		00	01	11	10
$A$	00	X	X	1	0
	01	X	0	0	0
	11	X	X	X	X
	10	0	0	0	0

$SB = A' \cdot B' \cdot x$

		$C$			
		00	01	11	10
$A$	00	X	X	0	X
	01	0	1	1	1
	11	X	X	X	X
	10	X	X	X	X

$RB = B \cdot C + B \cdot x$

## 6.4 Design: Example #3 (3/4)

- From state table, obtain expressions for flip-flop inputs (cont'd).

**$SC = x'$**

$AB \backslash Cx$	00	01	11	10
00	X	X	0	X
01	1	0	0	X
11	X	X	X	X
10	1	0	0	X

$x$

**$RC = x$**

$AB \backslash Cx$	00	01	11	10
00	X	X	1	0
01	0	X	1	0
11	X	X	X	X
10	0	X	1	0

$x$

$AB \backslash Cx$	00	01	11	10
00	X	X	0	0
01	0	0	0	0
11	X	X	X	X
10	0	1	1	0

$x$

**$y = A \cdot x$**

## 6.4 Design: Example #3 (4/4)

- From derived expressions, draw the logic diagram:

$$SA = B \cdot x$$

$$RA = C \cdot x'$$


$$SB = A' \cdot B' \cdot x$$

$$RB = B \cdot C + B \cdot x$$

$$SC = x'$$

$$RC = x$$

$$y = A \cdot x$$

 


# Self-Correcting Circuits (1/4)

- When a circuit has unused states, these unused states are considered to be “invalid”.
- Suppose we have a circuit with 2 flip-flops where states 0 to 2 are used. State 3 is unused and considered to be “invalid”.
- On the following pages we see two possible state diagrams for this circuit.



 
# Self-Correcting Circuits (2/4)

- Case 1: Non-self-correcting Circuit:
  - If the circuit finds itself in state 3 (e.g. due to a glitch), it will never transit into a valid state (state 0, 1, or 2).



- Case 2: **Self-Correcting Circuit**

 - A circuit that will (eventually) find its way back to a valid state.
- Here even if the circuit finds itself in state 3, it will transit to a valid state (either state 1 or 2)



# Self-Correcting Circuits (3/4)

- Is Design Example #3 self-correcting?
  - We recreate the state table for the invalid states and see if they lead to any valid states:

$$SA = B.x$$

$$SB = A'.B'.x$$

$$SC = x'$$

$$RA = C.x'$$

$$RB = B.C + B.x$$

$$RC = x$$

Valid states: 1, 2, 3, 4, 5.

Invalid states: 0, 6, 7.

(y is omitted since we don't need it to check for self-correction)

A	B	C	X	SA	RA	SB	RB	SC	RC	A+	B+	C+
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	1	0	1	0
1	1	0	0	0	0	0	0	1	0	1	1	1
1	1	0	1	1	0	0	1	0	1	1	0	0
1	1	1	0	0	1	0	1	1	0	0	0	1
1	1	1	1	1	0	0	1	0	1	1	0	0

# Self-Correcting Circuits (4/4)

- Is Design Example #3 self-correcting?
  - The transitions for the invalid states is summarized below:

ABC	(ABC)+	
	x=0	x=1
000	001	010
110	111	100
111	001	100

Valid states: 1, 2, 3, 4, 5.  
Invalid states: 0, 6, 7.

- We can see that every invalid state eventually transits to some valid state, hence this circuit is **self-correcting**.

**QnA Q2:**

Some of the tutorial qns require very long truth table + kmap which I feel is almost impossible to draw quickly during exam.

Any tips to be faster?

# QNA TOPIC 8



---

From previous semester:

Q7. hi prof, can you go through the memory array portion the  
4k x 8 ram portion
  
## 7.3 Memory Cell


- A single memory cell of the static RAM has the following logic and block diagrams:


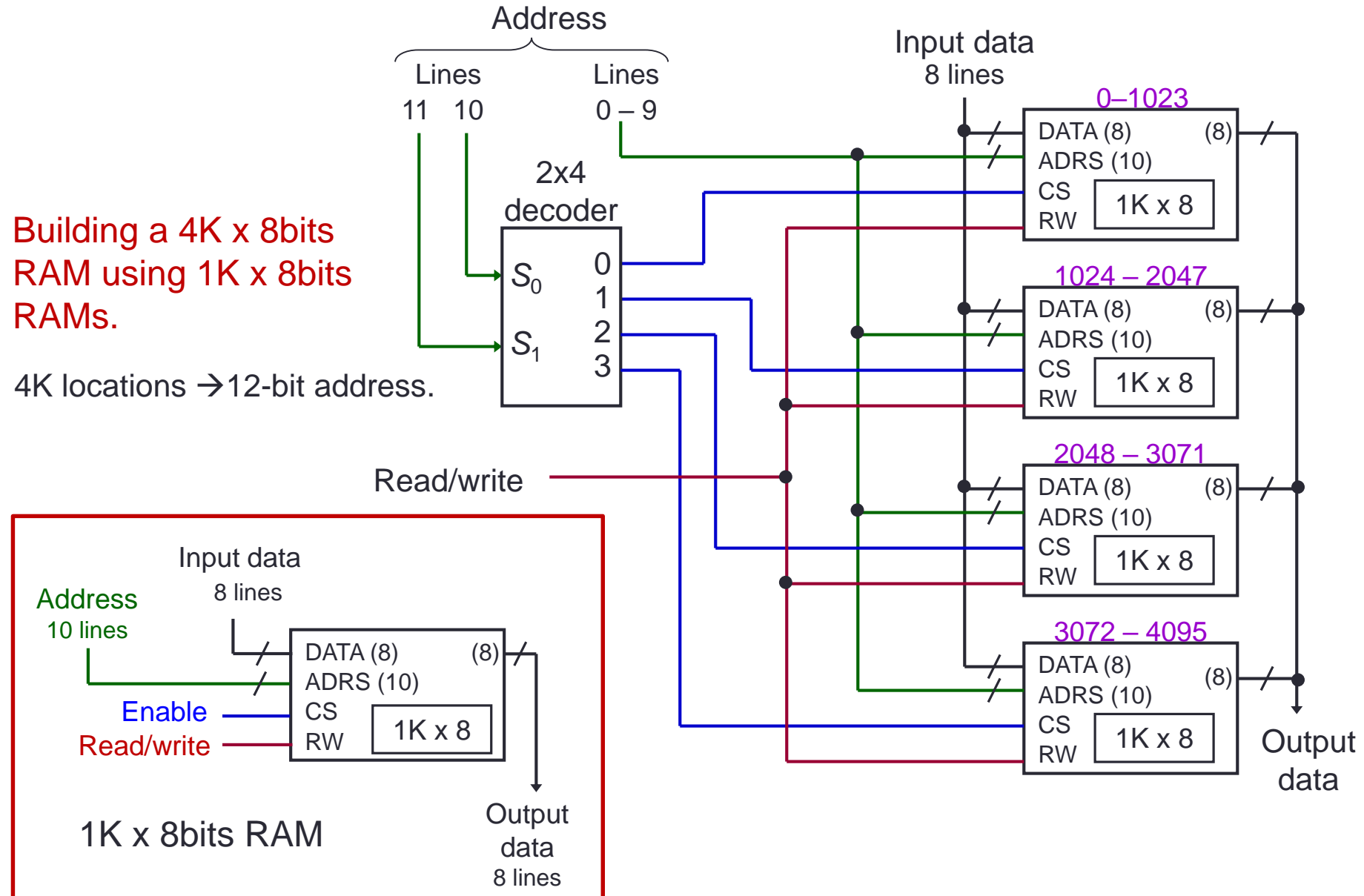
## 7.4 Memory Arrays (3/4)


Building a 4K x 8bits  
RAM using 1K x 8bits  
RAMs.

4K locations  $\rightarrow$  12-bit address.


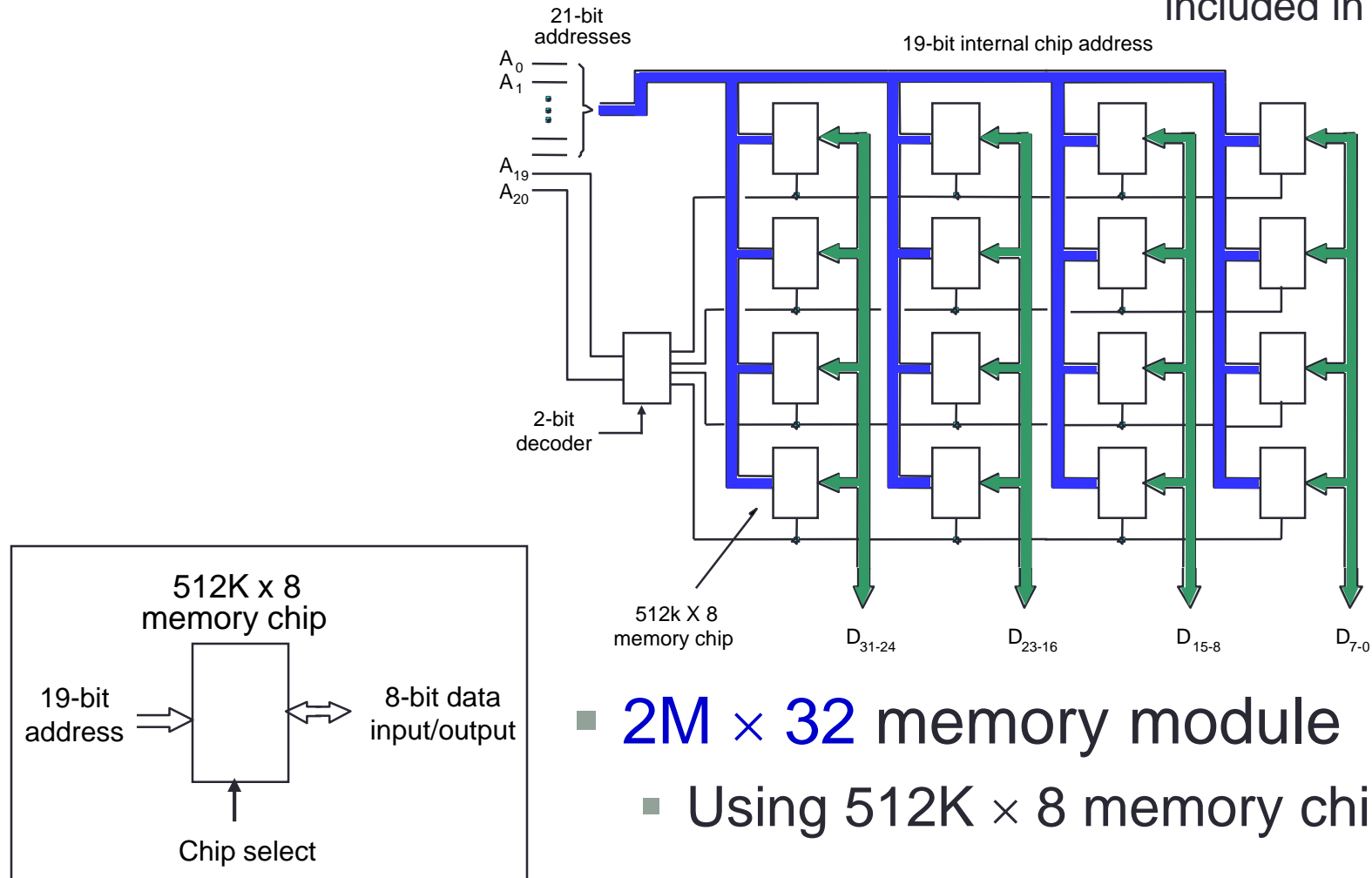
## 7.4 Memory Arrays (4/4)

Read/write control line not included in this diagram.



- **2M × 32** memory module
  - Using 512K × 8 memory chips.



# PAST YEARS' QUESTIONS

---


## Sequential Circuits

- AY2015/16 Sem1 Q7
- AY2020/21 Sem2 Q12

# AY2015/16 Sem1 Q7

 7. [8 marks]

A sequential circuit goes through the following states, whose state values are shown in decimal, as shown below:



The states are represented by 3-bit values  $ABC$ . Implement the sequential circuit using a  $JK$  flip-flop for  $A$ , a  $T$  flip-flop for  $B$ , and a  $D$  flip-flop for  $C$ .


- Write out the **simplified SOP expressions** for all the flip-flop inputs. Note that the simplified expression for  $KA$  has been done for you ( $KA = 0$ ). [3 marks]
- Complete the logic diagram on the answer booklet, by adding one inverter and a minimum number of logic gates of another type. [2 marks]
- Complete the given state diagram on the answer booklet, by indicating the next state for each of the two unused states. [2 marks]
- Is the circuit self-correcting? Explain your answer. (No mark will be awarded if there is no explanation or the explanation is wrong.) [1 mark]

# AY2015/16 Sem1 Q7

$Q$	$Q^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


$JK$  flip-flop  
excitation table

A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	JA	KA	TB	DC
0	0	0	0	0	1	0	X	0	1
0	0	1	0	1	0	0	X	1	0
0	1	0	0	1	1	0	X	0	1
0	1	1	1	0	0	1	X	1	0
1	0	0	1	0	1	X	0	0	1
1	0	1	1	0	1	X	0	0	1
1	1	0	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X

 


The states are represented by 3-bit values  $ABC$ . Implement the sequential circuit using a  $JK$  flip-flop for  $A$ , a  $T$  flip-flop for  $B$ , and a  $D$  flip-flop for  $C$ .

 
- a. Write out the **simplified SOP expressions** for all the flip-flop inputs. Note that the simplified expression for  $KA$  has been done for you ( $KA = 0$ ). [3 marks]



$$JA = B \cdot C$$

 

$$TB = A' \cdot C$$

 

$$DC = A + C'$$

$$KA = 0$$


# AY2015/16 Sem1 Q7

- b. Complete the logic diagram on the answer booklet, by adding one inverter and a minimum number of logic gates of another type. [2 marks]

$$JA = B \cdot C \quad TB = A' \cdot C \quad DC = A + C'$$

$$KA = 0$$

A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	JA	KA	TB	DC
0	0	0	0	0	1	0	X	0	1
0	0	1	0	1	0	0	X	1	0
0	1	0	0	1	1	0	X	0	1
0	1	1	1	0	0	1	X	1	0
1	0	0	1	0	1	X	0	0	1
1	0	1	1	0	1	X	0	0	1
1	1	0	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X

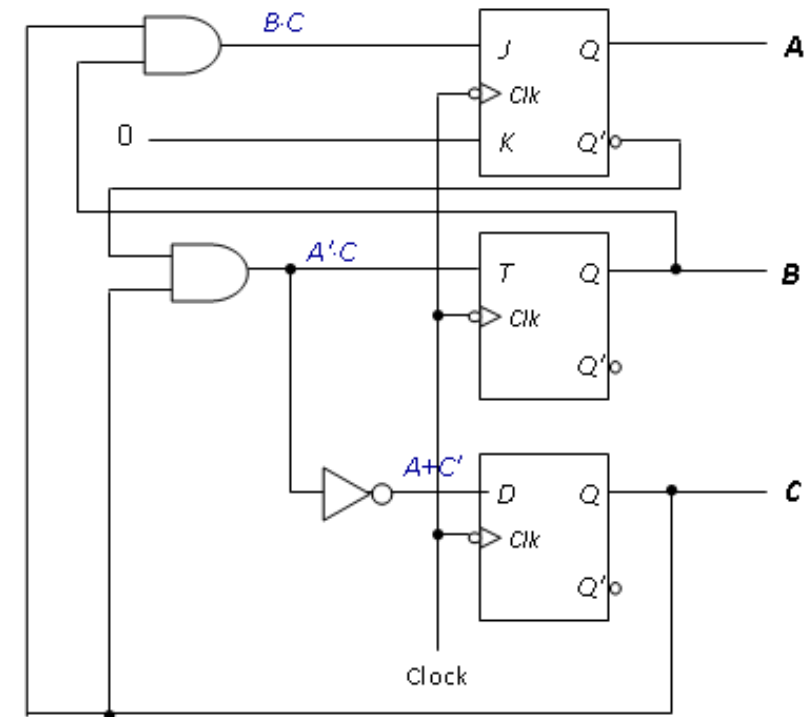


# AY2015/16 Sem1 Q7


- c. Complete the given state diagram on the answer booklet, by indicating the next state for each of the two unused states. [2 marks]

$$JA = B \cdot C \quad TB = A' \cdot C \quad DC = A + C'$$

$$KA = 0$$

 

A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	JA	KA	TB	DC
0	0	0	0	0	1	0	X	0	1
0	0	1	0	1	0	0	X	1	0
0	1	0	0	1	1	0	X	0	1
0	1	1	1	0	0	1	X	1	0
1	0	0	1	0	1	X	0	0	1
1	0	1	1	0	1	X	0	0	1
1	1	0	X(1)	X(1)	X(1)	X(0)	X(0)	X(0)	X(1)
1	1	1	X(1)	X(1)	X(1)	X(1)	X(0)	X(0)	X(1)

 


- d. Is the circuit self-correcting? Explain your answer. (No mark will be awarded if there is no explanation or the explanation is wrong.) [1 mark]

No

# AY2020/21 Sem2 Q12
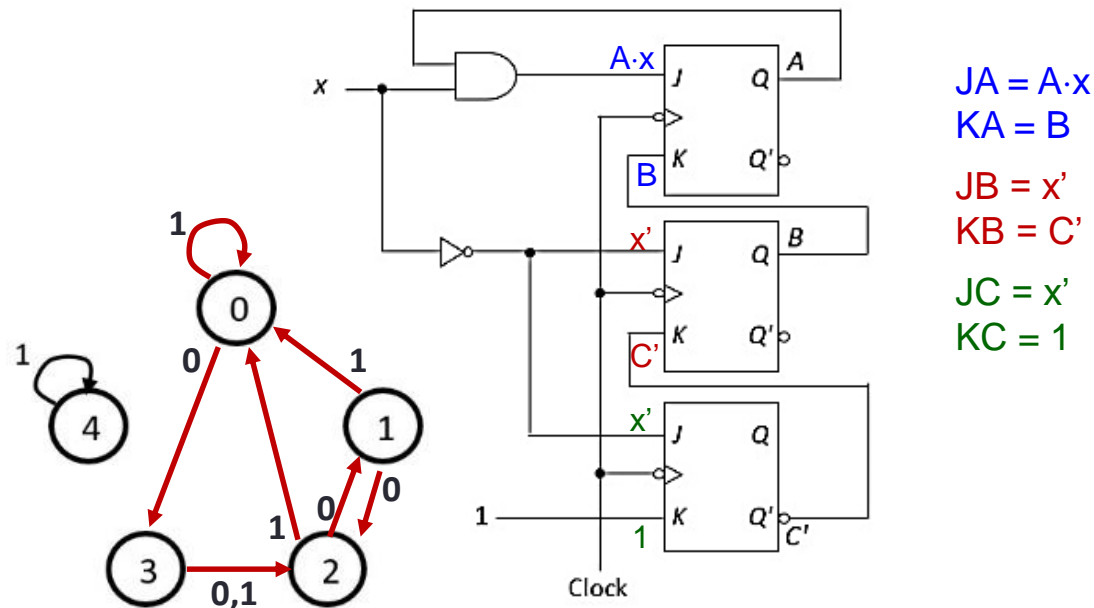
## Q12. Sequential circuits [12 marks]


Study the following sequential circuit with three JK flip-flops and an external input  $x$ . The states are represented by  $ABC$ . This circuit implements a machine with 5 valid states  $ABC = 000$  to  $100$  (or 0 to 4 in decimal). The other 3 states ( $ABC = 101$  to  $111$ , or 5 to 7 in decimal) are unused.



- (a) Complete the state diagram below by drawing the arrows and labelling each arrow with the value of  $x$ . States are shown in decimal values. You need only fill in the transitions to the used states 0, 1, 2, 3 and 4. You do not need to include the unused states 5, 6 and 7 in your diagram. The transition from state 4 has been drawn for you. [8]

A	B	C	x	JA	KA	JB	KB	JC	KC	A+	B+	C+
0	0	0	0	0	0	1	1	1	1	0	1	1
0	0	0	1	0	0	0	1	0	1	0	0	0
0	0	1	0	0	0	1	0	1	1	0	1	0
0	0	1	1	0	0	0	0	0	1	0	0	0
0	1	0	0	0	1	1	1	1	1	0	0	1
0	1	0	1	0	1	0	1	0	1	0	0	0
0	1	1	0	0	1	1	0	1	1	0	1	0
0	1	1	1	0	1	0	0	0	1	0	1	0
1	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	0	0	1	0	1	1	0	0
1	0	1	0	0	0	1	0	1	1	1	1	0
1	0	1	1	1	0	0	0	0	1	1	0	0
1	1	0	0	0	1	1	1	1	1	0	0	1
1	1	0	1	1	1	0	1	0	1	0	0	0
1	1	1	0	0	1	1	0	1	1	0	1	0
1	1	1	1	1	1	0	0	0	1	0	1	0

# AY2020/21 Sem2 Q12

 

$$JA = A \cdot x$$

$$KA = B$$

$$JB = x'$$

$$KB = C'$$


$$JC = x'$$

$$KC = 1$$

A	B	C	x	JA	KA	JB	KB	JC	KC	A+	B+	C+
0	0	0	0	0	0	1	1	1	1	0	1	1
0	0	0	1	0	0	0	1	0	1	0	0	0
0	0	1	0	0	0	1	0	1	1	0	1	0
0	0	1	1	0	0	0	0	0	1	0	0	0
0	1	0	0	0	1	1	1	1	1	0	0	1
0	1	0	1	0	1	0	1	0	1	0	0	0
0	1	1	0	0	1	1	0	1	1	0	1	0
0	1	1	1	0	1	0	0	0	1	0	1	0
1	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	0	0	1	0	1	1	0	0
1	0	1	0	0	0	1	0	1	1	1	1	0
1	0	1	1	1	0	0	0	0	1	1	0	0
1	1	0	0	0	1	1	1	1	1	0	0	1
1	1	0	1	1	1	0	1	0	1	0	0	0
1	1	1	0	0	1	1	0	1	1	0	1	0
1	1	1	1	1	1	0	0	0	1	0	1	0

# AY2020/21 Sem2 Q12

 - (b) If you did your state table correctly, you would see that state 4 is unreachable from any of the other used states 0, 1, 2 and 3. Redesign the above sequential circuit by removing state 4, using two D flip-flops to replace the 3 JK flip-flops. Call your flip flops  $F$  and  $G$ . Your circuit now has 4 used states  $FG = 00$  to  $11$  (or 0 to 3 in decimal). What are your flip-flop inputs  $DF$  and  $DG$ ? [4]



F	G	x	F <sup>+</sup>	G <sup>+</sup>
0	0	0	1	1
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

Note that  $Q^+ = D$  for D flip-flops.  
So  $F^+ = DF$  and  $G^+ = DG$ .

$DF$

	$G$			
	1	0	0	1
$F$	0	0	1	1
	$x$			

$$DF = F' \cdot x' + F \cdot G$$

$DG$

	$G$			
	1	0	0	0
$F$	1	0	0	0
	$x$			

$$DG = G' \cdot x'$$



End of File