

CS2100

<http://www.comp.nus.edu.sg/~cs2100/>

COMPUTER ORGANISATION

## Lecture #18

---

# MSI Components



**NUS**  
National University  
of Singapore

School of  
Computing



# Questions?

Ask at

<https://sets.netlify.app/module/676ca3a07d7f5ffc1741dc65>

**OR**

**Scan** and ask your questions here!  
(May be obscured in some slides)



# Lecture #18: MSI Components

1. Introduction
2. Decoders
3. Encoders
4. Demultiplexers
5. Multiplexers



# 1. Introduction (1/2)


- An **integrated circuit** (referred to as an **IC**, a **chip** or a **microchip**) is a set of electronic circuits on one small flat piece (or 'chip') of semiconductor material.
- **Scale of integration**: the number of components fitted into a standard size IC

Name	Signification	Year	#transistors	#logic gates
SSI	Small-scale integration	1964	1 to 10	1 to 12
MSI	Medium-scale integration	1968	10 to 500	13 to 99
LSI	Large-scale integration	1971	500 to 20000	100 to 9999
VLSI	Very large-scale integration	1980	20k to 1m	10k to 99999
ULSI	Ultra-large-scale integration	1984	1m and more	100k and more


 
# 1. Introduction (2/2)

- Four common and useful MSI circuits:
  - Decoder
  - Demultiplexer
  - Encoder
  - Multiplexer
- Block diagrams of the above MSI circuits:




## 2. Decoders (1/5)


- Codes are frequently used to represent entities, eg: your name is a code to denote yourself (an entity!)
- These codes can be identified (or decoded) using a decoder. Given a code, identify the entity.
- Convert binary information from  $n$  input lines to (a maximum of)  $2^n$  output lines.
- Known as  $n$ -to- $m$ -line decoder, or simply  $n:m$  or  $n \times m$  decoder ( $m \leq 2^n$ ).
- May be used to generate  $2^n$  minterms of  $n$  input variables.



# Decoding – the inefficient way

 


# Decoding – the better way

 



## 2. Decoders (2/5)

 - Example: If codes 00, 01, 10, 11 are used to identify four light bulbs, we may use a 2-bit decoder.



- This is a **2×4 decoder** which selects an output line based on the 2-bit code supplied.
- Truth table:


X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	<b>1</b>	0	0	0
0	1	0	<b>1</b>	0	0
1	0	0	0	<b>1</b>	0
1	1	0	0	0	<b>1</b>



## 2. Decoders (3/5)

- From truth table, circuit for **2×4 decoder** is:
- Note: Each output is a minterm ( $X' \cdot Y'$ ,  $X' \cdot Y$ ,  $X \cdot Y'$  or  $X \cdot Y$ ) of a 2-variable function


X	Y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	<b>1</b>	0	0	0
0	1	0	<b>1</b>	0	0
1	0	0	0	<b>1</b>	0
1	1	0	0	0	<b>1</b>

 

## 2. Decoders (4/5)


- Design a **3×8 decoder**.

x	y	z	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>
0	0	0	<b>1</b>	0	0	0	0	0	0	0
0	0	1	0	<b>1</b>	0	0	0	0	0	0
0	1	0	0	0	<b>1</b>	0	0	0	0	0
0	1	1	0	0	0	<b>1</b>	0	0	0	0
1	0	0	0	0	0	0	<b>1</b>	0	0	0
1	0	1	0	0	0	0	0	<b>1</b>	0	0
1	1	0	0	0	0	0	0	0	<b>1</b>	0
1	1	1	0	0	0	0	0	0	0	<b>1</b>

 
 
## 2. Decoders (5/5)

- In general, for an  $n$ -bit code, a decoder could select up to  $2^n$  lines:



## 2. Decoders: Implementing Functions (1/3)

- A Boolean function, in **sum-of-minterms** form  $\Rightarrow$ 
  - decoder to generate the minterms, and
  - an OR gate to form the sum.
- Any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n:2^n$  decoder with  $m$  OR gates.
- Good when circuit has many outputs, and each function is expressed with a few minterms.




## 2. Decoders: Implementing Functions (2/3)

- Example: Full adder

$$S(x, y, z) = \Sigma m(1,2,4,7)$$

$$C(x, y, z) = \Sigma m(3,5,6,7)$$


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

## 2. Decoders: Implementing Functions (3/3)

$$S(x, y, z) = \Sigma m(1,2,4,7)$$

$$C(x, y, z) = \Sigma m(3,5,6,7)$$

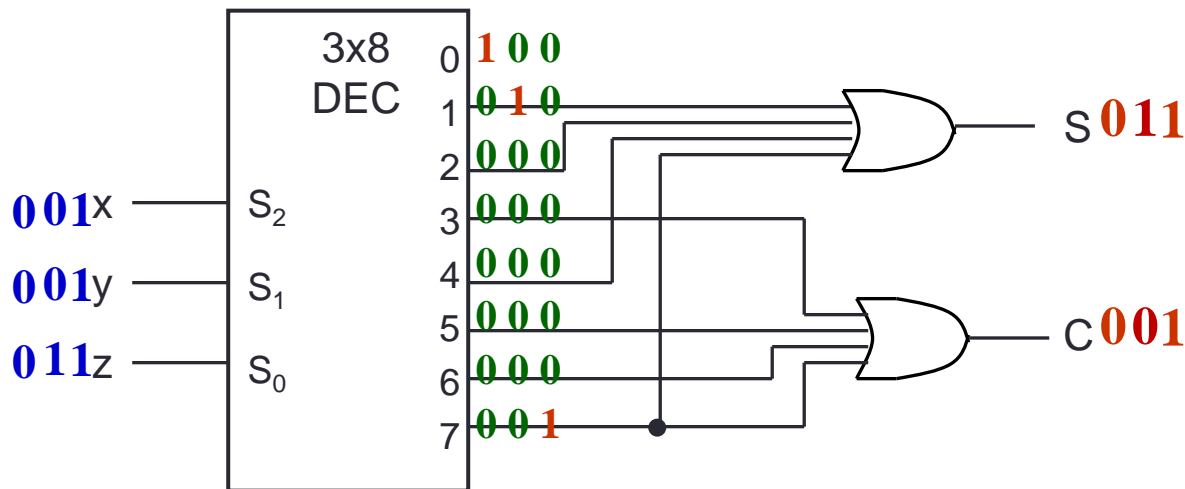

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

**BRAVO!!!**




## 2. Decoders with Enable (1/2)

- Decoders often come with an **enable control** signal, so that the device is only activated when the enable,  $E = 1$ .

- Truth table:

E	X	Y	$F_0$	$F_1$	$F_2$	$F_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	d	d	0	0	0	0

 - Circuit of a **2×4 decoder with enable**:





## 2. Decoders with Enable (2/2)

- In the previous slide, the decoder has a **one-enable** control signal, i.e. the decoder is enabled with  $E=1$ .
- In most MSI decoders, enable signal is **zero-enable**, usually denoted by  $E'$  or  $\bar{E}$ . The decoder is enabled when the signal is zero (low).

E	X	Y	$F_0$	$F_1$	$F_2$	$F_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	d	d	0	0	0	0

Decoder with 1-enable



$E'$	X	Y	$F_0$	$F_1$	$F_2$	$F_3$
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	d	d	0	0	0	0

Decoder with 0-enable



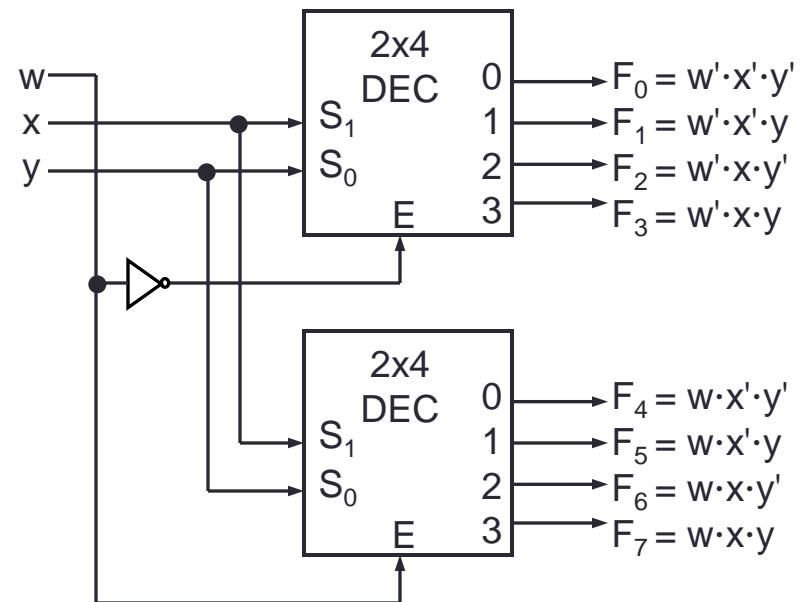
 
## 2. Constructing Larger Decoders (1/4)

- Larger decoders can be constructed from smaller ones.
- Example: A 3×8 decoder can be built from two 2×4 decoders (with one-enable) and an inverter.





## 2. Constructing Larger Decoders (2/4)

**BRAVO!!!**

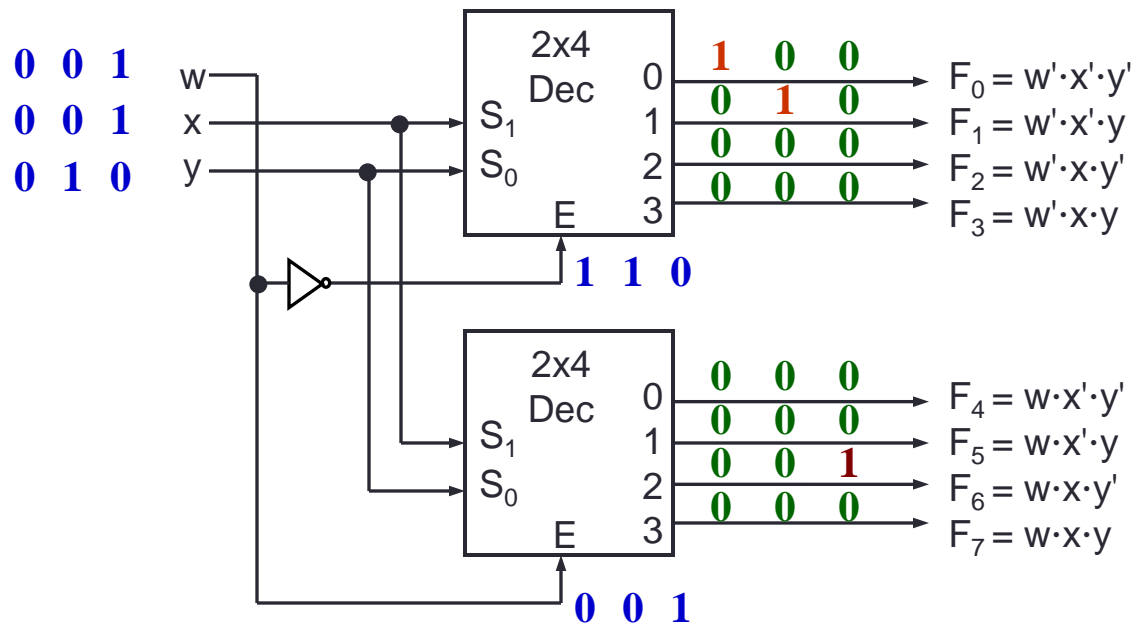 
  
## 2. Constructing Larger Decoders (3/4)

- Construct a 4×16 decoder from two 3×8 decoders with one-enable and an inverter.



- Note: The input  $w$  and its complement  $w'$  are used to select either one of the two smaller decoders.





## 2. Constructing Larger Decoders (4/4)

- **Exercise:** What modifications should be made to provide an ENABLE input for the  $3 \times 8$  decoder and the  $4 \times 16$  decoder created in the previous two examples?
- **Exercise:** How to construct a  $4 \times 16$  decoder using five  $2 \times 4$  decoders with enable?
- Decoders may also have **zero-enable** and/or **negated outputs**. (See next two slides.)
  - Normal outputs = active high outputs
  - Negated outputs = active low outputs



## 2. Standard MSI Decoder (1/2)

### ■ 74138 (3-to-8 decoder)

  

74138 decoder module.

(a) Logic circuit.

(b) Package pin configuration.



## 2. Standard MSI Decoder (2/2)

INPUTS					OUTPUTS							
ENABLE		SELECT										
G1	$\overline{G2}^*$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	L	H	H	H	H
H	L	H	L	H	H	H	H	L	H	H	H	H
H	L	H	H	L	H	H	H	H	L	H	H	H
H	L	H	H	H	H	H	H	H	H	L	H	H

74138 decoder module.  
(c) Function table.

$$*\overline{G2} = \overline{G2A} + \overline{G2B}$$

H = high level, L = low level, X = irrelevant


(c)

74138 decoder module.


(d) Generic symbol.

 (e) IEEE standard logic symbol.

Source: *The Data Book Volume 2, Texas Instruments Inc., 1985*



(d)

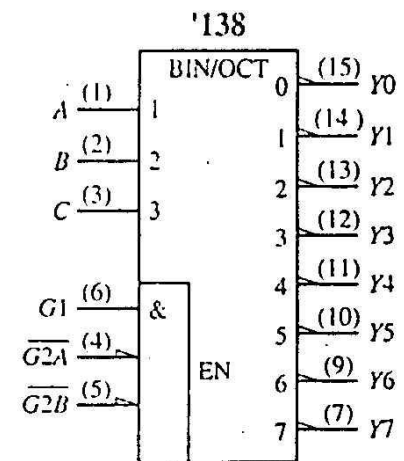

(e)



## 2. Decoders: Implementing Functions Revisit (1/2)

- Example: Implement the following function using a 3×8 decoder and an appropriate logic gate

$$f(Q,X,P) = \sum m(0,1,4,6,7) = \prod M(2,3,5)$$


- We may implement the function in several ways:
  - Using a decoder with active-high outputs with an OR gate:
$$f(Q,X,P) = m_0 + m_1 + m_4 + m_6 + m_7$$
  - Using a decoder with active-low outputs with a NAND gate:
$$f(Q,X,P) = (m_0' \cdot m_1' \cdot m_4' \cdot m_6' \cdot m_7')'$$
  - Using a decoder with active-high outputs with a NOR gate:
$$f(Q,X,P) = (m_2 + m_3 + m_5)' [= M_2 \cdot M_3 \cdot M_5]$$
  - Using a decoder with active-low outputs with an AND gate:
$$f(Q,X,P) = m_2' \cdot m_3' \cdot m_5'$$





 
## 2. Decoders: Implementing Functions Revisit (2/2)


$$f(Q,X,P) = \sum m(0,1,4,6,7) = \prod M(2,3,5)$$




(a) Active-high decoder with OR gate.

 

(b) Active-low decoder with NAND gate.

 

(c) Active-high decoder with NOR gate.

 

(d) Active-low decoder with AND gate.




# Reading

- **Reducing Decoders**
  - Read up DLD pages 136 – 140.



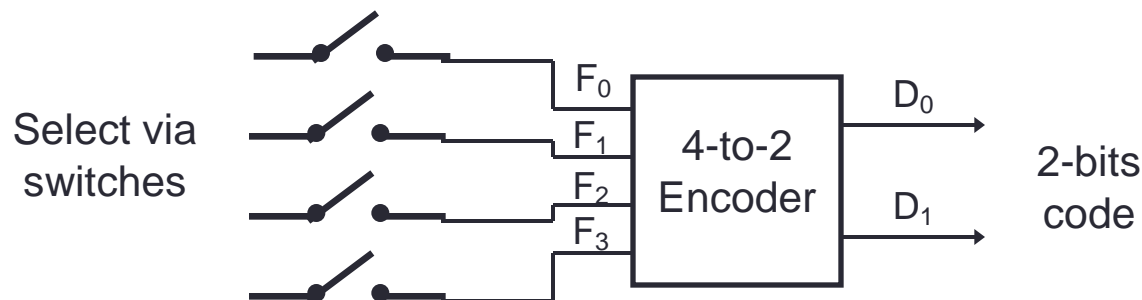
### 3. Encoders (1/4)


- **Encoding** is the converse of decoding.
- Given a set of input lines, of which exactly one is high and the rest are low, the **encoder** provides a code that corresponds to that high input line.
- Contains  $2^n$  (or fewer) input lines and  $n$  output lines.
- Implemented with OR gates.
- Example:



# Encoding – the inefficient way

 


# Encoding – the better way

 

### 3. Encoders (2/4)

- Truth table:
- With K-map, we obtain:
  - $D_0 = F_1 + F_3$
  - $D_1 = F_2 + F_3$
- Circuit:

 

Simple 4-to-2 encoder

$F_0$	$F_1$	$F_2$	$F_3$	$D_1$	$D_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1
0	0	0	0	X	X
0	0	1	1	X	X
0	1	0	1	X	X
0	1	1	0	X	X
0	1	1	1	X	X
1	0	0	1	X	X
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X



## 3. Encoders (3/4)


- Example: 8-to-3 encoder.
  - At any one time, only one input line of an encoder has a value of 1 (high), the rest are zeroes (low).
  - To allow for more than one input line to carry a 1, we need **priority encoder**.

Inputs								Outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1



### 3. Encoders (4/4)

- Example: 8-to-3 encoder.

 

An 8-to-3 encoder

- Exercise:** Can you design a  $2^n$ -to- $n$  encoder without using K-map?





### 3. Priority Encoders (1/2)

- A **priority encoder** is one with priority
  - If two or more inputs are equal to 1, the input with the highest priority takes precedence.
  - If all inputs are 0, this input combination is considered invalid.
- Example of a **4-to-2 priority encoder**:

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$f$	$g$	$v$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1



## 3. Priority Encoders (2/2)

- Understanding “compact” function table

Inputs				Outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	f	g	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1


Inputs				Outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	f	g	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
0	1	0	0	0	1	1
1	1	0	0	0	1	1
0	0	1	0	1	0	1
0	1	1	0	1	0	1
1	0	1	0	1	0	1
1	1	1	0	1	0	1
0	0	0	1	1	1	1
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

- Exercise:** Obtain the simplified expressions for  $f$ ,  $g$  and  $V$ .



# Multiplexers and Demultiplexers

- An application:

 


- Helps share a *single communication line* among a number of devices.
- At any time, only one source and one destination can use the communication line.


 
## 4. Demultiplexers (1/2)

- Given an input line and a set of selection lines, a **demultiplexer** directs data from the input to one selected output line.
- Example: **1-to-4 demultiplexer**.





S <sub>1</sub>	S <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D



  
## 4. Demultiplexers (2/2)

- It turns out that the demultiplexer circuit is actually identical to a decoder with enable.


 
## 5. Multiplexers (1/4)

- A **multiplexer** is a device that has
  - A number of input lines
  - A number of selection lines
  - One output line
- It steers one of  $2^n$  inputs to a single output line, using  $n$  selection lines. Also known as a **data selector**.





## 5. Multiplexers (2/4)

- Truth table for a **4-to-1 multiplexer**:

$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
$d_0$	$d_1$	$d_2$	$d_3$	0	0	$d_0$
$d_0$	$d_1$	$d_2$	$d_3$	0	1	$d_1$
$d_0$	$d_1$	$d_2$	$d_3$	1	0	$d_2$
$d_0$	$d_1$	$d_2$	$d_3$	1	1	$d_3$

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

  

## 5. Multiplexers (3/4)

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

- Output of multiplexer is  
“sum of the (product of *data lines* and *selection lines*)”
- Example: Output of a 4-to-1 multiplexer is:

$$Y = I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$

*Note:*

Expressing

$$I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$

in minterms notation, it is equal to

$$I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3$$



This is useful later (eg: slide 45).





  
## 5. Multiplexers (4/4)

- A  $2^n$ -to-1-line multiplexer, or simply  $2^n:1$  MUX, is made from an  $n:2^n$  decoder by adding to it  $2^n$  input lines, one to each AND gate.
- A **4:1 multiplexer circuit:**



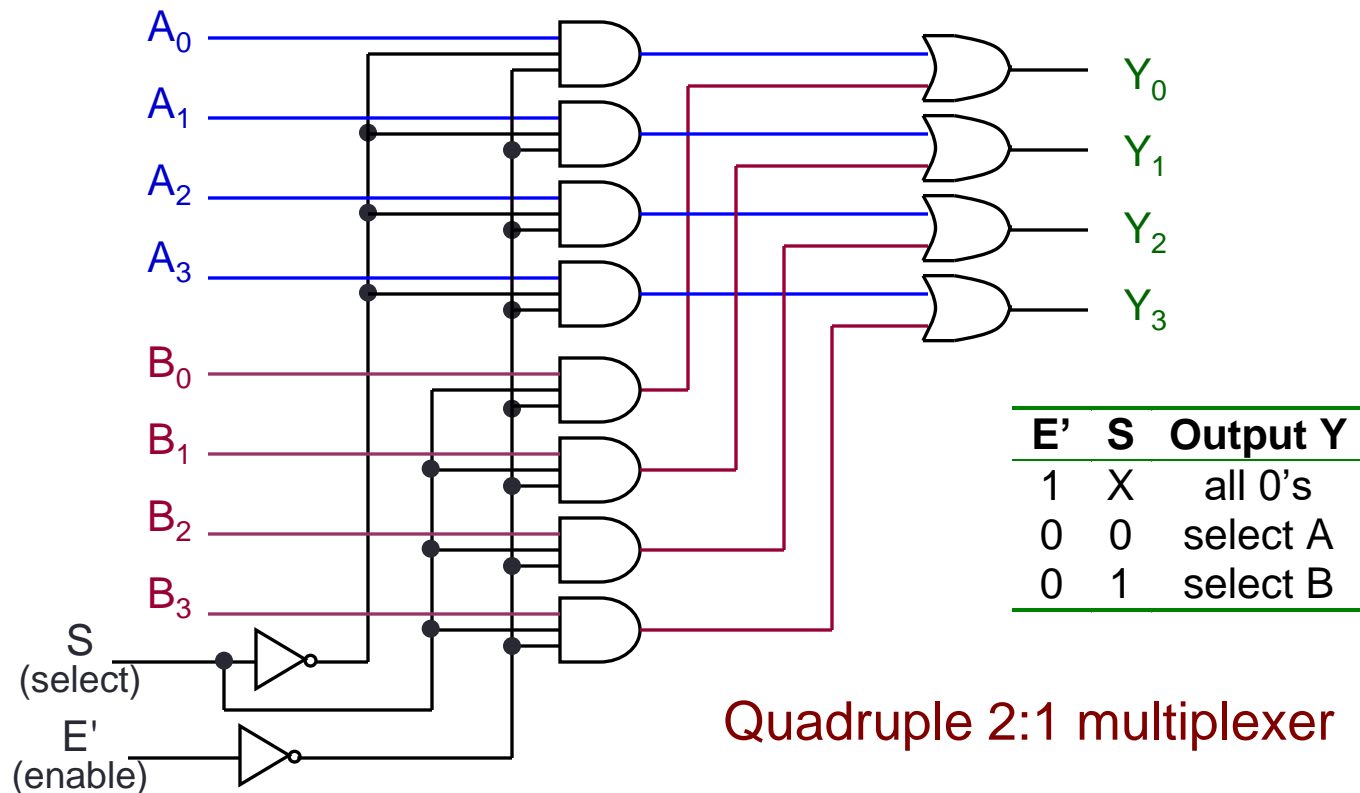
## 5. Multiplexer IC Package

- Some IC packages have a few multiplexers in each package (chip). The selection and enable inputs are common to all multiplexers within the package.


 
## 5. Constructing Larger Multiplexers (1/4)


- Larger multiplexers can be constructed from smaller ones.
- An 8-to-1 multiplexer can be constructed from smaller multiplexers like this (note placement of selector lines):



$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$


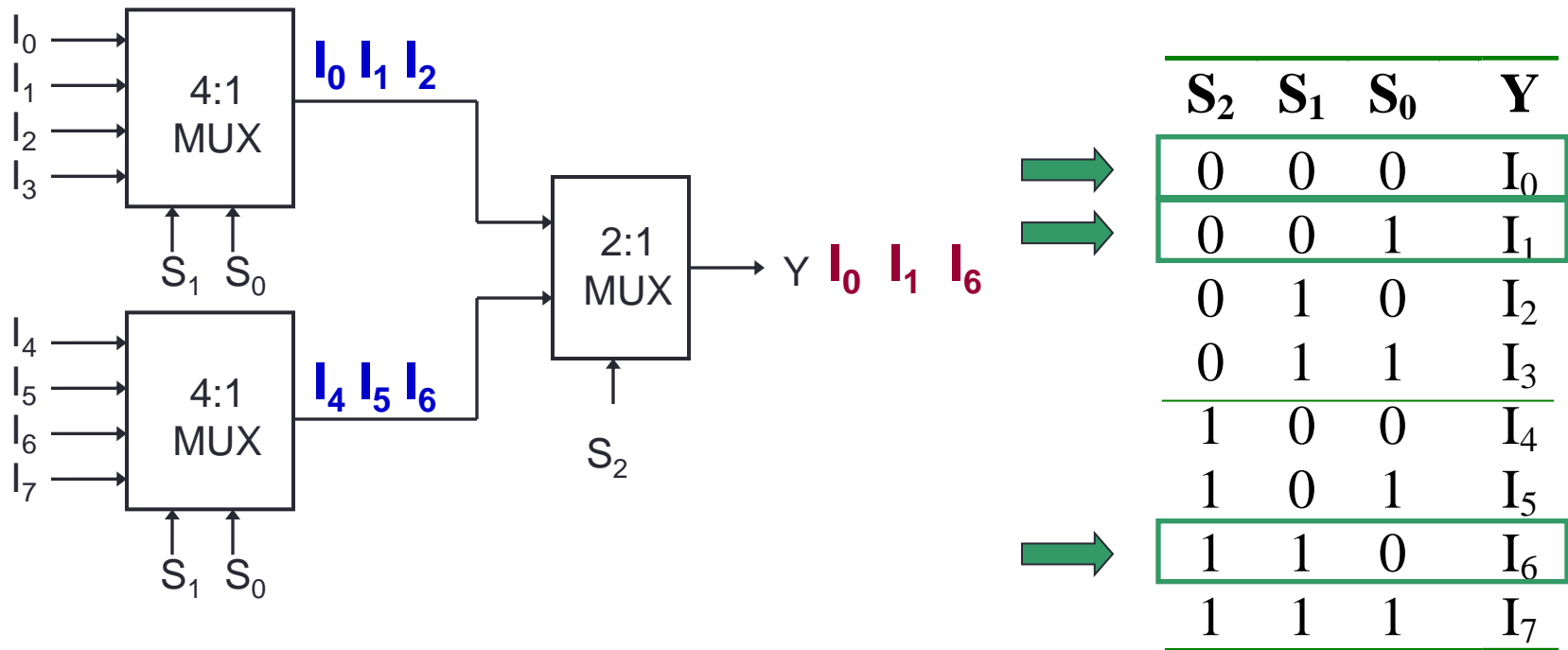
## 5. Constructing Larger Multiplexers (2/4)




- When  $S_2 S_1 S_0 = 000$
- When  $S_2 S_1 S_0 = 001$
- When  $S_2 S_1 S_0 = 110$



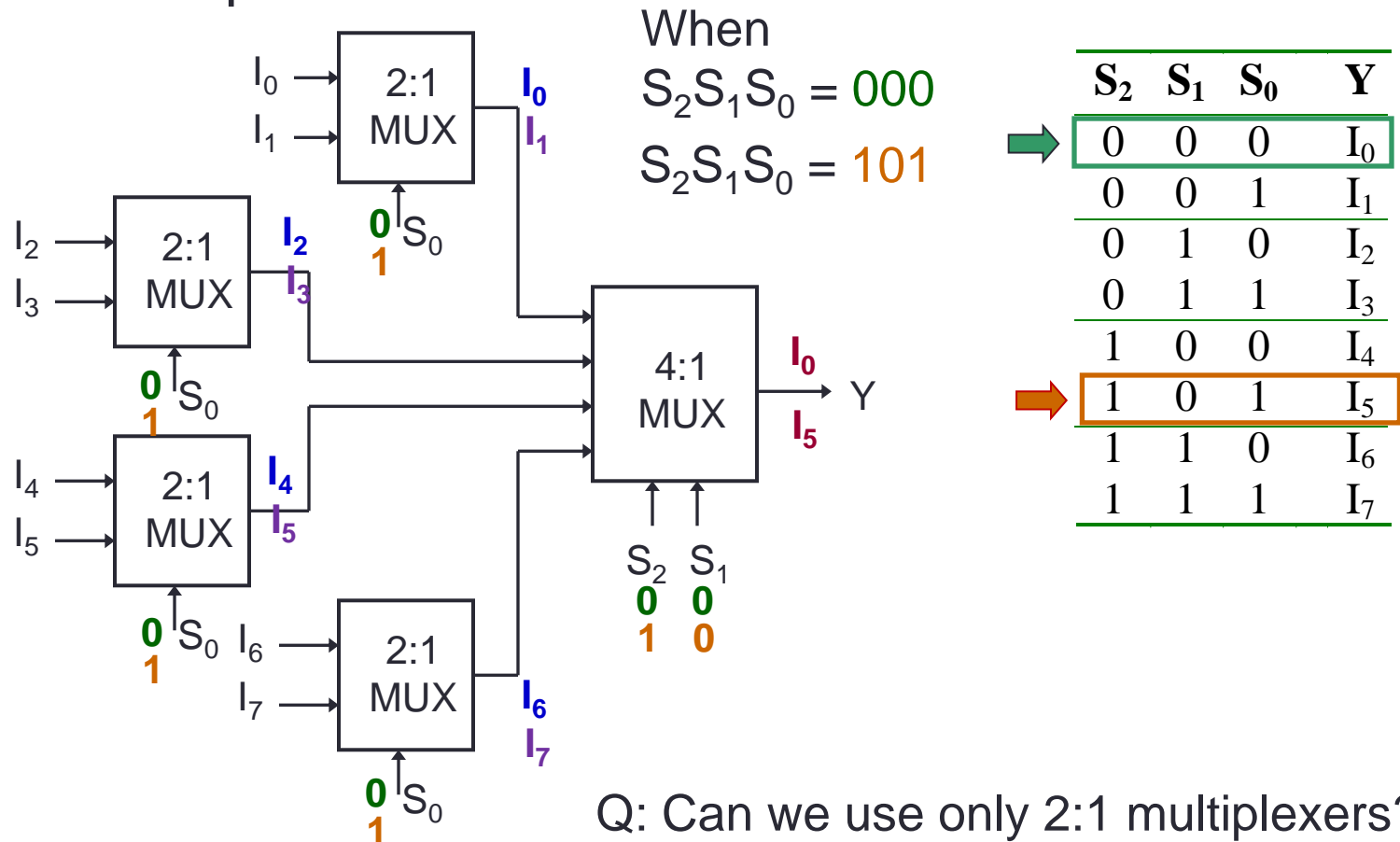
## 5. Constructing Larger Multiplexers (3/4)

- Another implementation of an **8-to-1 multiplexer** using smaller multiplexers:



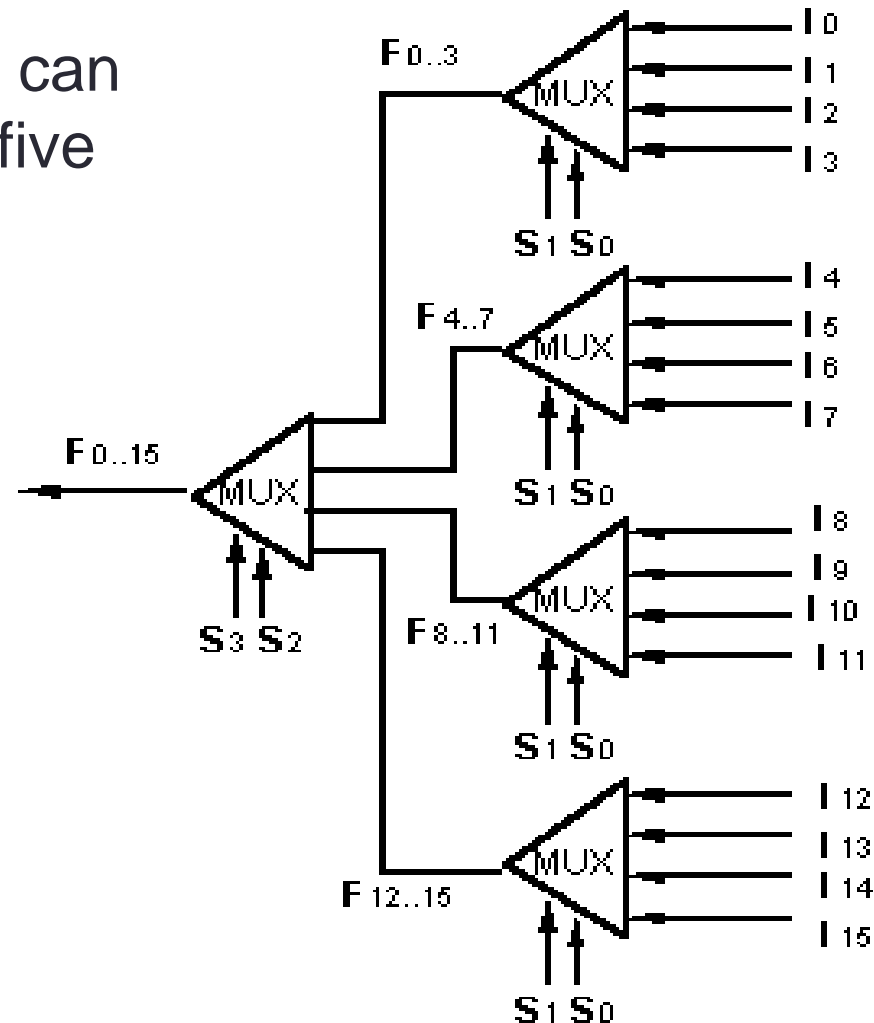
## 5. Constructing Larger Multiplexers (4/4)

- A 16-to-1 multiplexer can be constructed from five 4-to-1 multiplexers:



## 5. Standard MSI Multiplexer (1/2)

 




INPUTS				OUTPUTS	
SELECT			STROBE $\overline{G}$	Y	W
C	B	A			
X	X	X	H	L	H
L	L	L	L	D0	$\overline{D0}$
L	L	H	L	D1	$\overline{D1}$
L	H	L	L	D2	$\overline{D2}$
L	H	H	L	D3	$\overline{D3}$
H	L	L	L	D4	$\overline{D4}$
H	L	H	L	D5	$\overline{D5}$
H	H	L	L	D6	$\overline{D6}$
H	H	H	L	D7	$\overline{D7}$

(b)

**74151A 8-to-1 multiplexer.** (a) Package configuration. (b) Function table.



## 5. Standard MSI Multiplexer (2/2)

  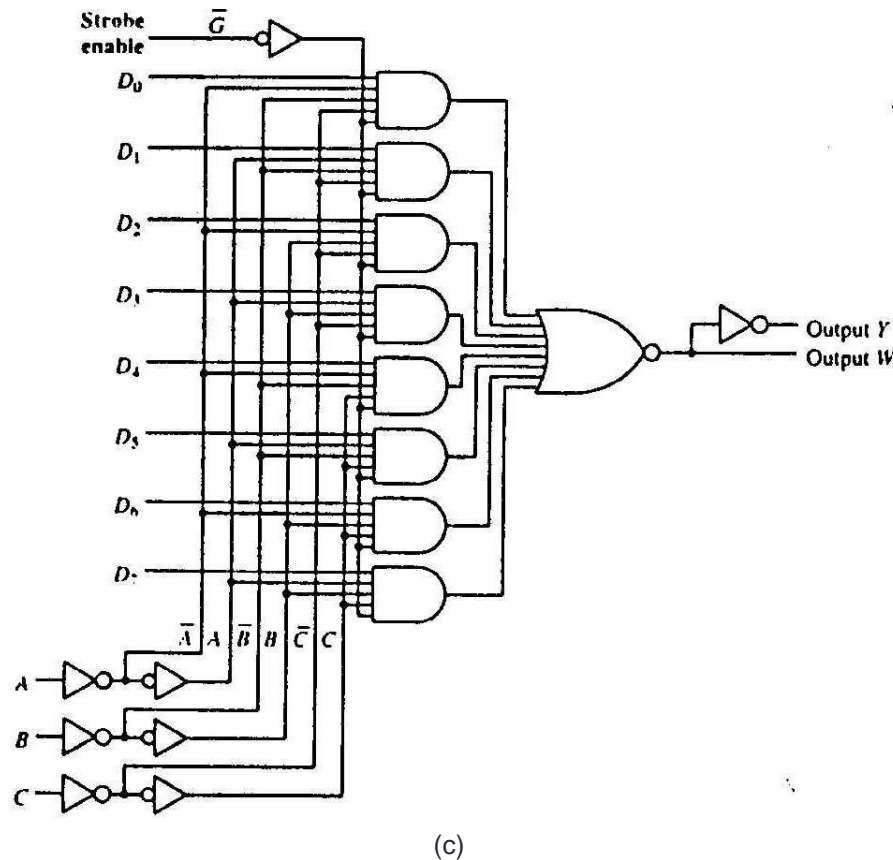

**74151A 8-to-1 multiplexer.** (c) Logic diagram. (d) Generic logic symbol.  
(e) IEEE standard logic symbol.

Source: *The TTL Data Book Volume 2. Texas Instruments Inc., 1985.*





## 5. Multiplexers: Implementing Functions (1/3)

- Boolean functions can be implemented using multiplexers.
- A  $2^n$ -to-1 multiplexer can implement a Boolean function of  $n$  input variables, as follows:

1. Express in sum-of-minterms form.

Example:


$$\begin{aligned} F(A,B,C) &= A' \cdot B' \cdot C + A' \cdot B \cdot C + A \cdot B' \cdot C + A \cdot B \cdot C' \\ &= \Sigma m(1,3,5,6) \end{aligned}$$

2. Connect  $n$  variables to the  $n$  selection lines.
3. Put a '1' on a data line if it is a minterm of the function, or '0' otherwise.



## 5. Multiplexers: Implementing Functions (2/3)

■  $F(A,B,C) = \Sigma m(1,3,5,6)$

 

This method works because:

$$\text{Output} = I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3 \\ + I_4 \cdot m_4 + I_5 \cdot m_5 + I_6 \cdot m_6 + I_7 \cdot m_7$$

Supplying '1' to  $I_1, I_3, I_5, I_6$ , and '0' to the rest:

$$\text{Output} = m_1 + m_3 + m_5 + m_6$$

From slide 34 (4:1 mux)

Expressing

$$I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0)$$

in minterms notation, it is equal to

$$I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3$$

## 5. Multiplexers: Implementing Functions (3/3)

- Example: Use a 74151A to implement  

$$f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$$


$i$	$C$	$B$	$A$	$Y$
	$x_1$	$x_2$	$x_3$	$f$
0	0	0	0	1 $D_0 = 1$
1	0	0	1	0 $D_1 = 0$
2	0	1	0	1 $D_2 = 1$
3	0	1	1	1 $D_3 = 1$
4	1	0	0	0 $D_4 = 0$
5	1	0	1	1 $D_5 = 1$
6	1	1	0	0 $D_6 = 0$
7	1	1	1	0 $D_7 = 0$

(a)

Realization of  $f(x_1, x_2, x_3) = \sum m(0, 2, 3, 5)$ .

(a) Truth table.

(b) Implementation with 74151A.

 

(b)



## 5. Using Smaller Multiplexers (1/6)



- Earlier, we saw how a  $2^n$ -to-1 multiplexer can be used to implement a Boolean function of  $n$  (input) variables.
- However, we can use a single smaller  $2^{(n-1)}$ -to-1 multiplexer to implement a Boolean function of  $n$  (input) variables.
- Example: The function
$$F(A,B,C) = \Sigma m(1,3,5,6)$$
can be implemented using a 4-to-1 multiplexer (rather than an 8-to-1 multiplexer).


  
## 5. Using Smaller Multiplexers (2/6)

- Let's look at this example:

$$F(A,B,C) = \sum m(0,1,3,6) = A' \cdot B' \cdot C' + A' \cdot B' \cdot C + A' \cdot B \cdot C + A \cdot B \cdot C'$$



- Note: Two of the variables, **A** and **B**, are applied as selection lines of the multiplexer, while the inputs of the multiplexer contain **1**, **C**, **0** and **C'**.



## 5. Using Smaller Multiplexers (3/6)

### ■ Procedure

1. Express Boolean function in sum-of-minterms form.

Example:  $F(A,B,C) = \sum m(0,1,3,6)$

2. Reserve one variable (in our example, we take the least significant one) for input lines of multiplexer, and use the rest for selection lines.


Example:  $C$  is for input lines;  $A$  and  $B$  for selection lines.



## 5. Using Smaller Multiplexers (4/6)

3. Draw the truth table for function, by grouping inputs by selection line values, then determine multiplexer inputs by comparing input line (**C**) and function (**F**) for corresponding selection line values.


A	B	C	F	MUX input
0	0	0	1	<b>1</b>
0	0	1	1	
0	1	0	0	<b>C</b>
0	1	1	1	
1	0	0	0	<b>0</b>
1	0	1	0	
1	1	0	1	<b>C'</b>
1	1	1	0	

 

## 5. Using Smaller Multiplexers (5/6)

- Alternative: What if we use **A** for input lines, and **B**, **C** for selector lines?

A	B	C	F	Mux Input
0	0	0	1	1
0	0	1	1	
0	1	0	0	C
0	1	1	1	
1	0	0	0	0
1	0	1	0	
1	1	0	1	C'
1	1	1	0	

 

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$A'$  (when  $BC = 00$ )

$A'$  (when  $BC = 01$ )

$A$  (when  $BC = 10$ )

$A'$  (when  $BC = 11$ )






## 5. Using Smaller Multiplexers (6/6)

- Example: Implement the function below with 74151A:

$$f(x_1, x_2, x_3, x_4) = \Sigma m(0, 1, 2, 3, 4, 9, 13, 14, 15)$$

	C B A						Y
i	X <sub>1</sub>	X <sub>2</sub>	X <sub>3</sub>	X <sub>4</sub>	f	f	
0	0	0	0	0	1		
	0	0	0	1	1	1	$D_0 = 1$
1	0	0	1	0	1	1	$D_1 = 1$
	0	0	1	1	1	1	
2	0	1	0	0	1		
	0	1	0	1	0	$\bar{X}_4$	$D_2 = \bar{X}_4$
3	0	1	1	0	0		
	0	1	1	1	0	0	$D_3 = 0$
4	1	0	0	0	0		
	1	0	0	1	1	$X_4$	$D_4 = X_4$
5	1	0	1	0	0		
	1	0	1	1	0	0	$D_5 = 0$
6	1	1	0	0	0		
	1	1	0	1	1	$X_4$	$D_6 = X_4$
7	1	1	1	0	1		
	1	1	1	1	1	1	$D_7 = 1$


(a)

 

(b)



# Peeking Ahead

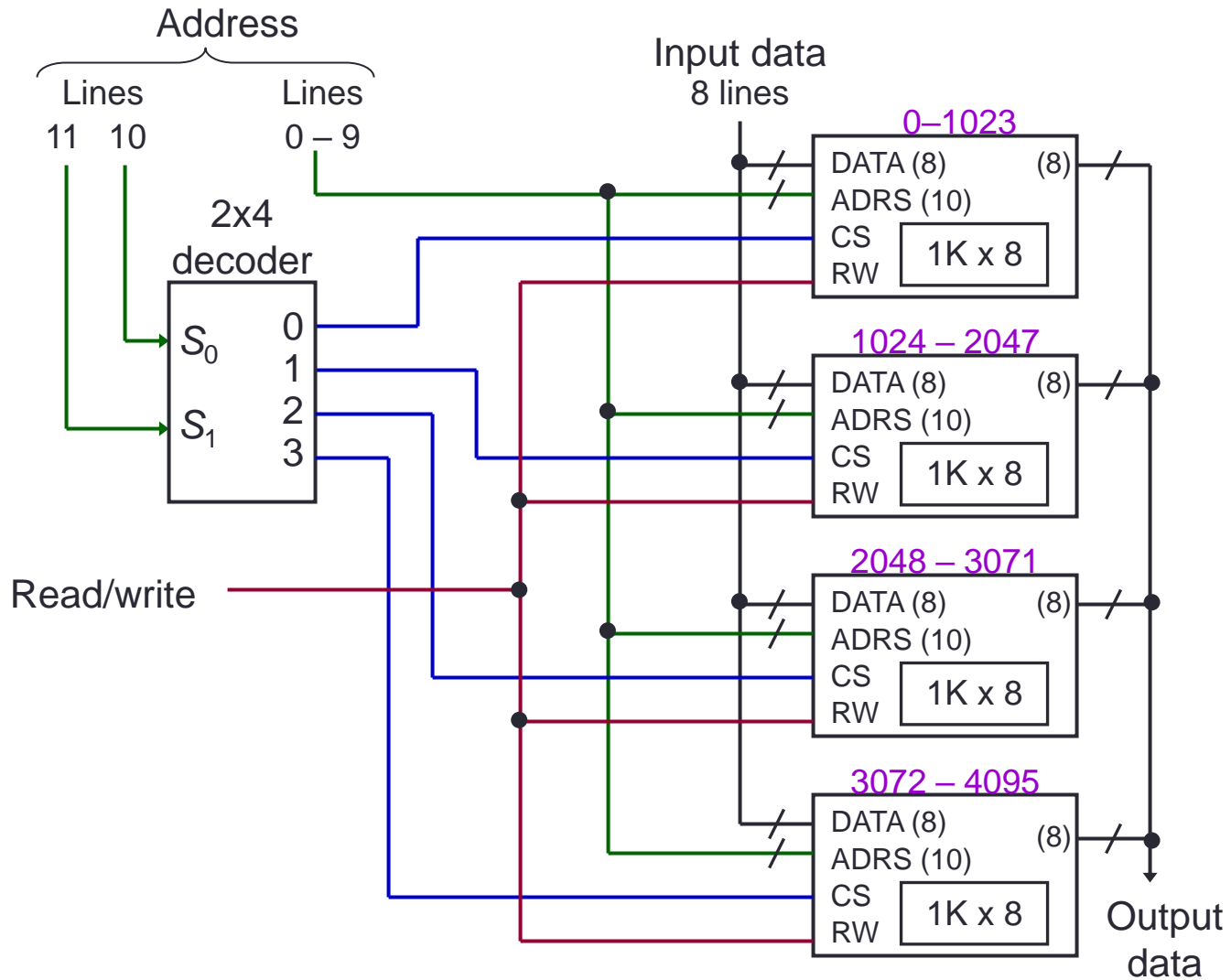

# End of File

